

# **Block I**

## **Apollo Guidance Computer (AGC)**

**How to build one in your basement**

**Part 3: Processing (PROC) Module**

John Pultorak  
December, 2004

## Abstract

This report describes my successful project to build a working reproduction of the 1964 prototype for the Block I Apollo Guidance Computer. The AGC is the flight computer for the Apollo moon landings, and is the world's first integrated circuit computer.

I built it in my basement. It took me 4 years.

If you like, you can build one too. It will take you less time, and yours will be better than mine.

I documented my project in 9 separate .pdf files:

- Part 1**      **Overview:** Introduces the project.
- Part 2**      **CTL Module:** Design and construction of the control module.
- Part 3**      **PROC Module:** Design and construction of the processing (CPU) module.
- Part 4**      **MEM Module:** Design and construction of the memory module.
- Part 5**      **IO Module:** Design and construction of the display/keyboard (DSKY) module.
- Part 6**      **Assembler:** A cross-assembler for AGC software development.
- Part 7**      **C++ Simulator:** A low-level simulator that runs assembled AGC code.
- Part 8**      **Flight Software:** My translation of portions of the COLOSSUS 249 flight software.
- Part 9**      **Test & Checkout:** A suite of test programs in AGC assembly language.

# Overview

The Processing Module (PROC) has 5 subsystems: PMI, ALU, CRG, INT, CTR

## PMI (Processing Module external Interface)

The PMI interfaces other processing module subsystems to external AGC modules. 40-pin IDE connectors interface to the other CTL, MEM, and IO modules. Inputs from those modules are buffered to 1 LSTTL load.

## ALU (Arithmetic Logic Unit)


The ALU contains the 16-bit ADDER to perform 1's complement arithmetic and increment the program counter (Z register). The ALU also contains the B and C registers, and logic to inclusive OR the contents of the them with the ADDER. The inclusive OR occurs when the control module (CTL) issues signals to READ the contents of both registers onto the READ bus simultaneously. The ALU transfers data from the READ bus to the WRITE bus for register-to-register transfers and can force the data lines of the WRITE bus to specific states to gate various constants into the AGC registers

## CRG (Central Register)

The AGC has four 16-bit "central registers" for general computational use. These are the accumulator (A) for general computation; the program counter (Z) which contains the address of the next instruction; the Q register holding the remainder in the DV instruction, and the return address after TC instructions; and the LP register used to hold the lower product after MP instructions.
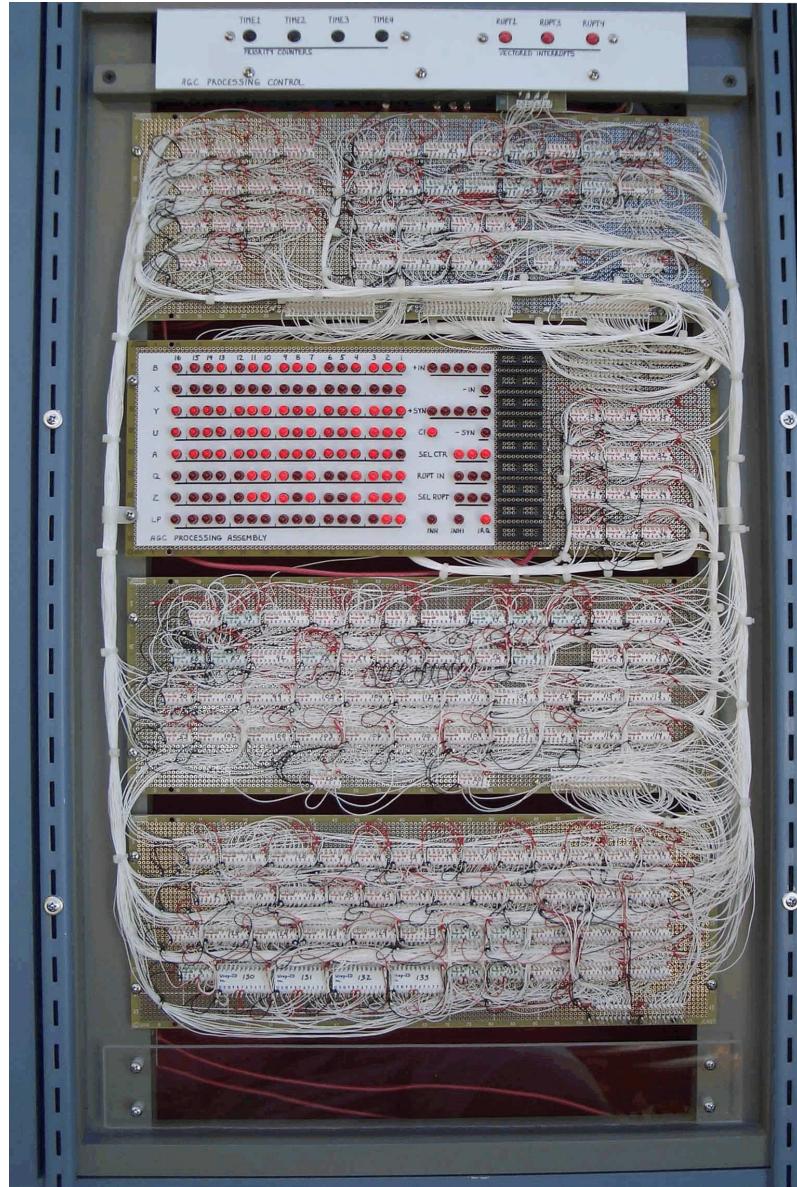
## INT (Interrupt Priority)


The original AGC had five vectored interrupts. This recreation implements three of them: RUPT1, also called T3RUPT which is used as general-purpose timer by the AGC WAITLIST software; RUPT3, also called T4RUPT or DSRUPT, which is used to update the DSKY display at regular intervals; and RUPT4, also called KERUPT, which is triggered by a key press from the user's keyboard. The AGC responds to each interrupt by temporarily suspending the current program, executing a short interrupt service routine, and then resuming the



interrupted program.
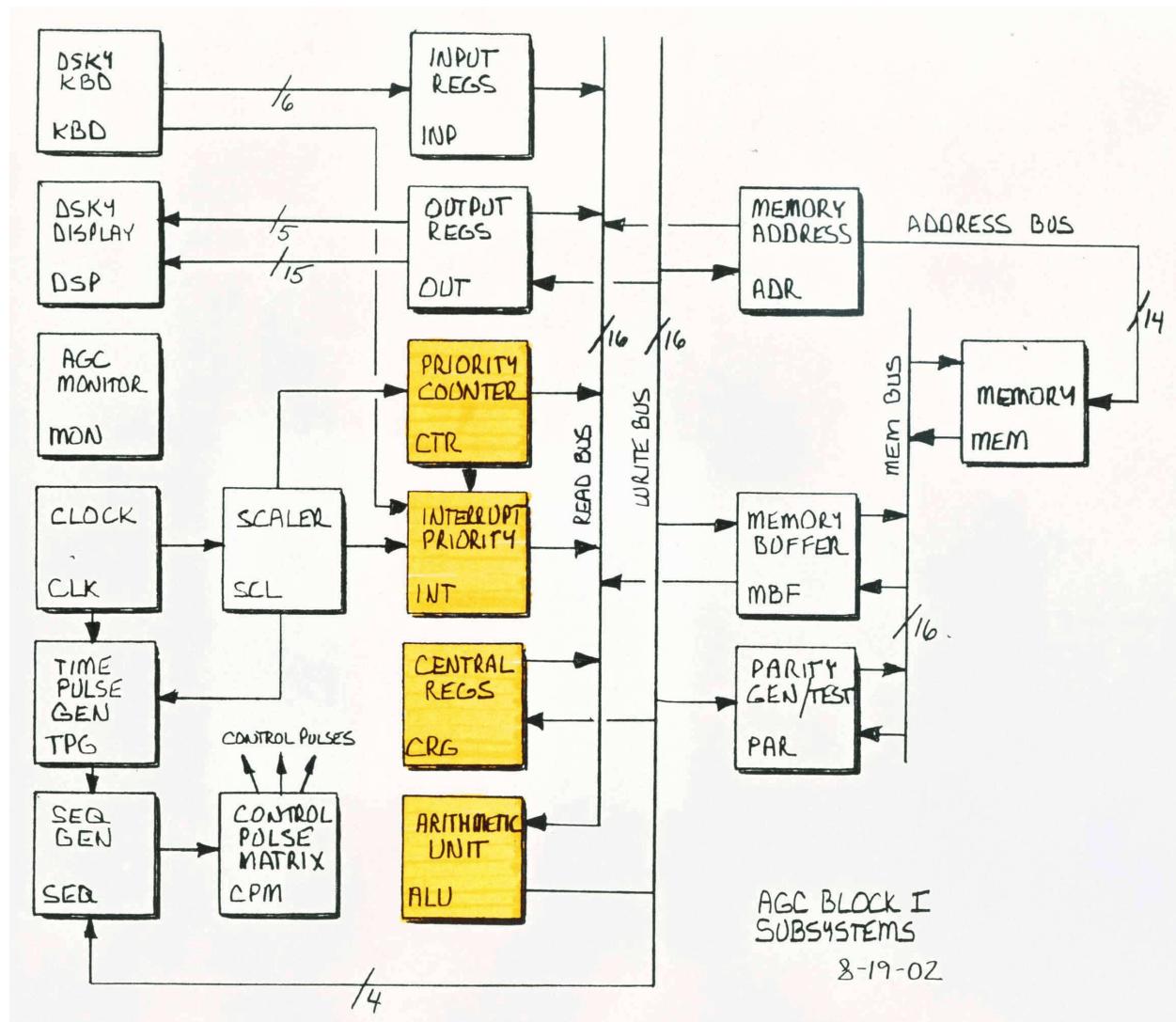
### CTR (Priority Counter)

Twenty memory locations in the original AGC functioned as up/down counters. The counters would increment (PINC) or decrement (MINC) in response to external inputs. Increment or decrement was handled by one 12-step subsequence of microinstructions inserted between any two regular instructions. This replica implements 5 of the counters: OVCTR, an overflow counter incremented or decremented by arithmetic overflow during certain instructions; TIME2 and TIME1, the AGC real-time clock; TIME3, a general purpose timer incremented by a 100Hz signal from the SCALER (SCL); and TIME4, a timer used to update the DSKY display.




The ALU has a 16-bit parallel adder. The addend and augend are supplied by the X and Y registers. The sum, called the U register although it is not really a register at all, is gated to the read bus through the RU (read U) control signal. The WX and WY control signals copy the contents of the write bus into the X and Y registers.

The B register is loaded from the write bus with the WB (write B) signal. The contents of B are output to the read bus with the RB (read B) signal. The inverted output of B can be gated to the read bus with the RC (read C) signal.

NOTE: ALSO INCLUDES MANY CONTROL PULSES FOR SETTING SUBSETS OF BITS ON THE R/W BUS.

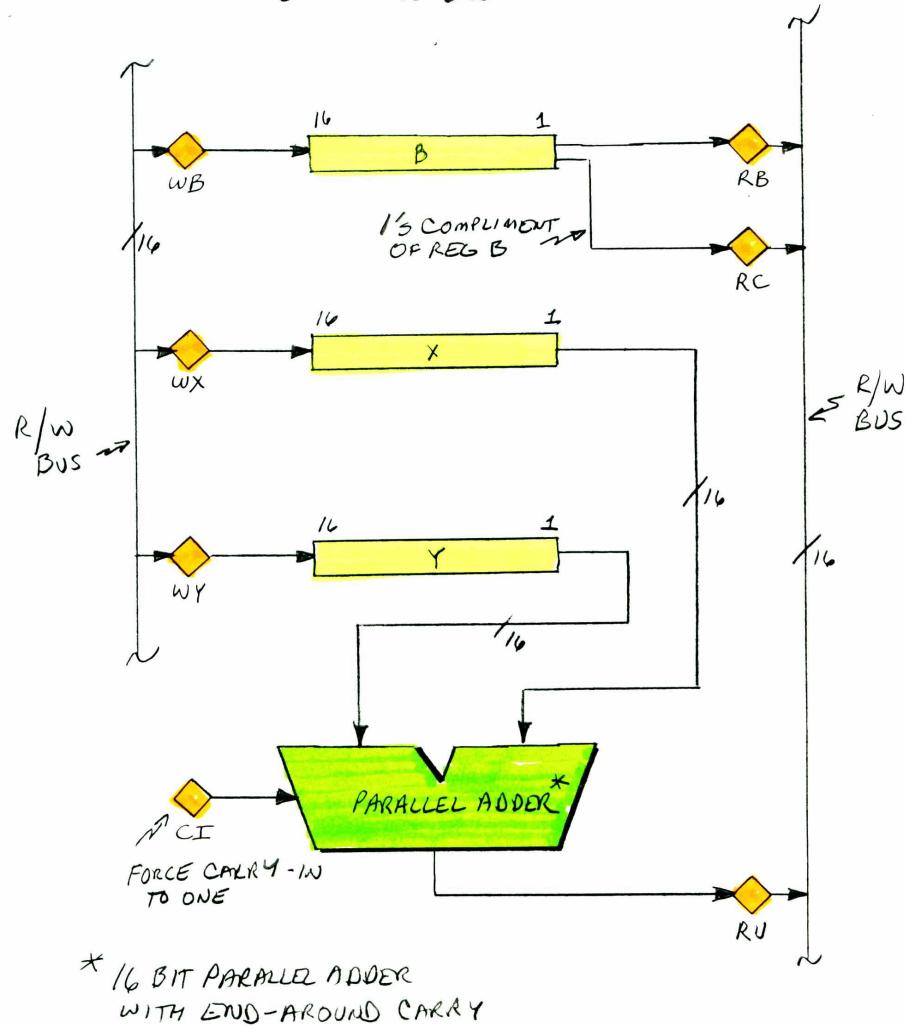
MOST READ PULSES ARE INCLUSIVE OR'ED ON TO THE BUS.



The AGC has four user-accessible central registers. The A register is the accumulator; Z is the program counter; Q stores the return address for jumps (TC instruction), and LP stores the lower product (MP instruction).

Central register contents can be output to the read bus by asserting the appropriate read control pulse (RA, RQ, RZ, or RLP). Each register is also mapped to a memory location, with register A mapped to address 0, Q to address 1, Z to 2, and LP to 3. The R0, R1, R2, and R3 control pulses output those registers to the read bus.

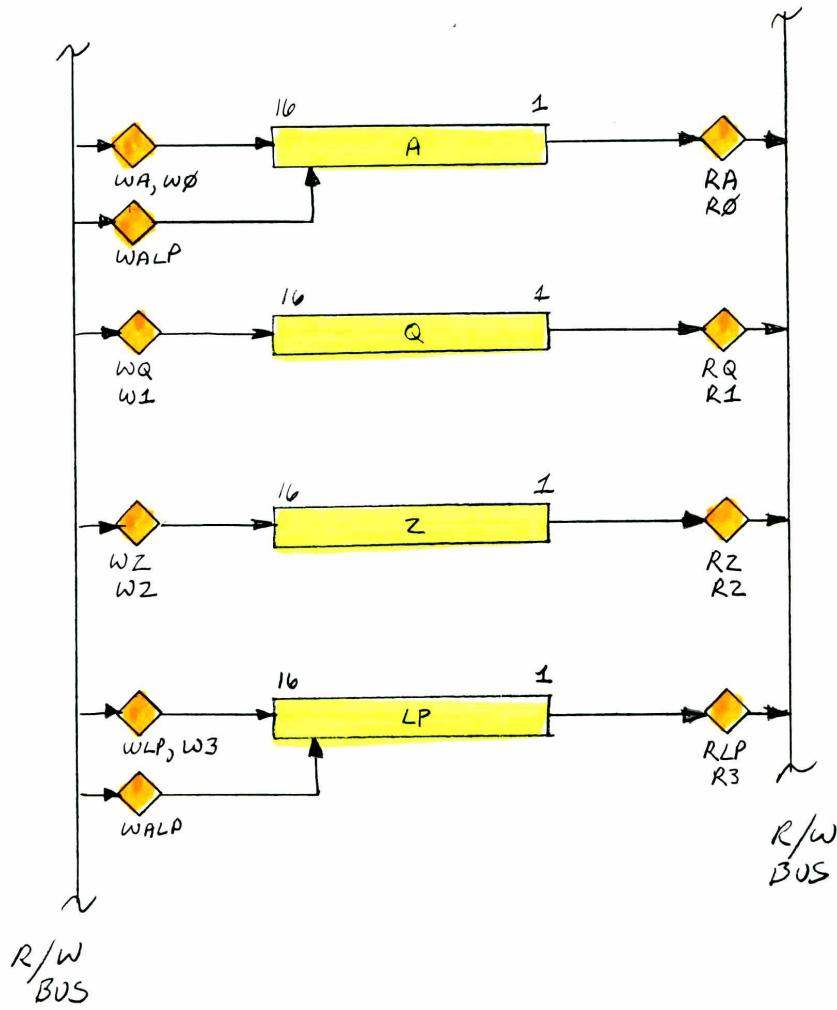
The write bus contents can be loaded into a central register with a write control pulse. WA and WALP load the A register; WQ, the Q register; WZ the Z register; and WLP and WALP the LP register. The W0, W1, W2, and W3 control pulses mapped to memory addresses 0,1,2, and 3 also load those registers.



The interrupt priority subsystem manages vectored interrupts. Five interrupts (0-4) are implemented. Each interrupt is latched by its own "RP cell" flip-flop. Signals from all RP cells feed into a priority encoder; a combinational logic array that outputs the code of the highest priority interrupt in the RP cells. When RPT is asserted, the priority code is latched into RPCELL. This is decoded into an address which is the interrupt vector; the address is written to the read bus when RRPA is asserted.

After the interrupt code has been loaded into RPCELL, asserting KRPT (knock-down RPT) causes the RP cell for that interrupt to be reset. This causes the next highest priority interrupt to be decoded by the priority encoder.

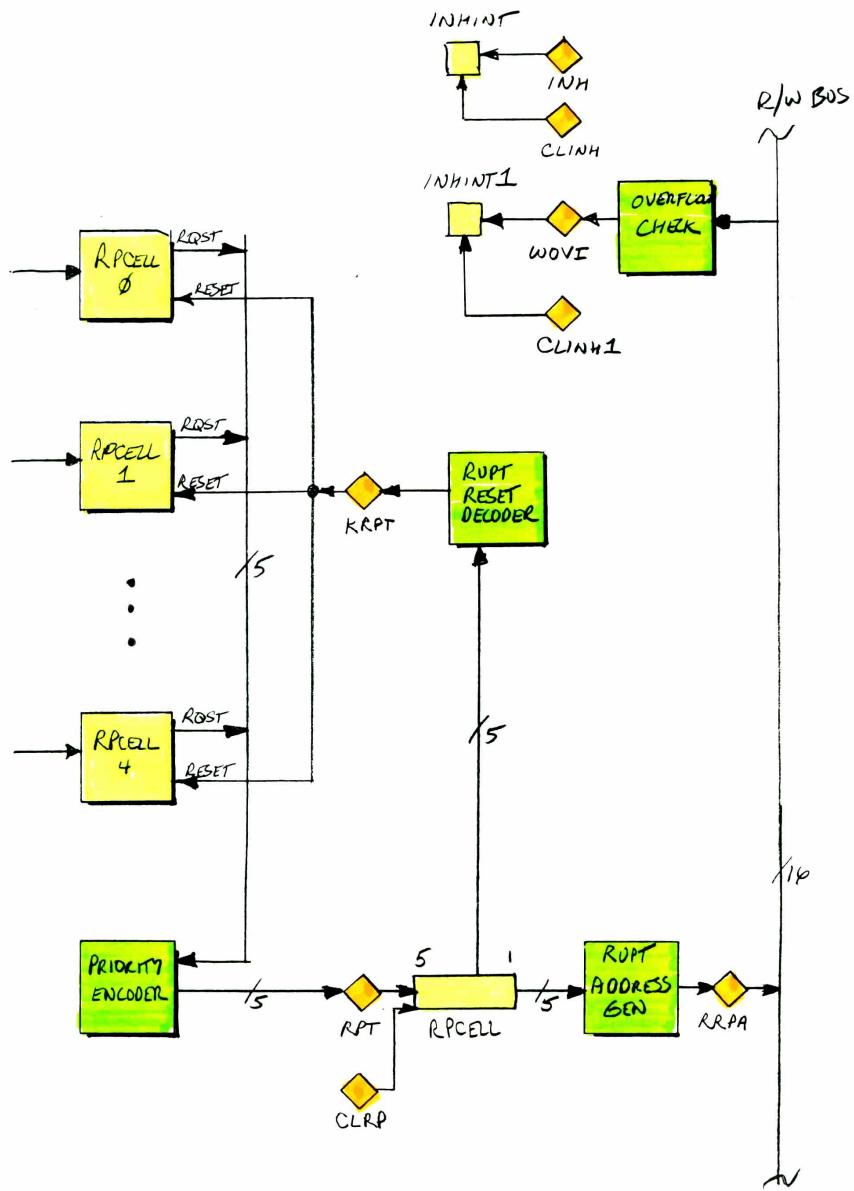The INHINT and INHINT1 flip-flops inhibit interrupts.




The priority counter logic design is similar to the interrupt subsystem. Up (+) and down (-) count input signals feed into 20 PCELLs, one PCELL for each counter. The PCELLs feed into the priority encoder which outputs the code of the highest priority PCELL having a up or down input set. The PCELL code is written to the PCELL register when WPCTR is asserted.

The PCELL memory address, derived from PCELL, is written to read bus when RSCT is asserted. After the code is latched into the PCELL register, the corresponding PCELL is reset by asserting WOVR.


The up or down code for the selected PCELL is written to PSEQ when WPCTR is asserted. This code feeds to the control logic on the CTL module which selects the PINC (increment) or MINC (decrement) instruction subsequence to bump the priority counter up or down.

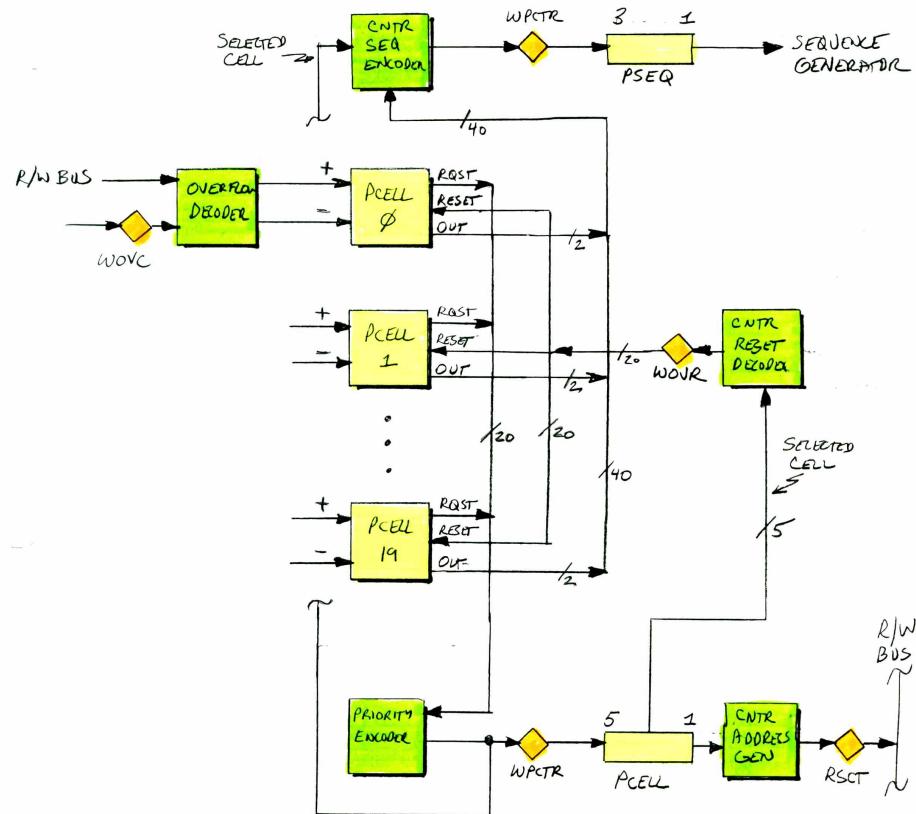The PINC and MINC subsequences are inserted between normal instruction subsequences. A SHINC subsequence implements a bit-shift which is used to load telemetry bits into the AGC and assemble them into words. SHINC is not implemented in this AGC replica.


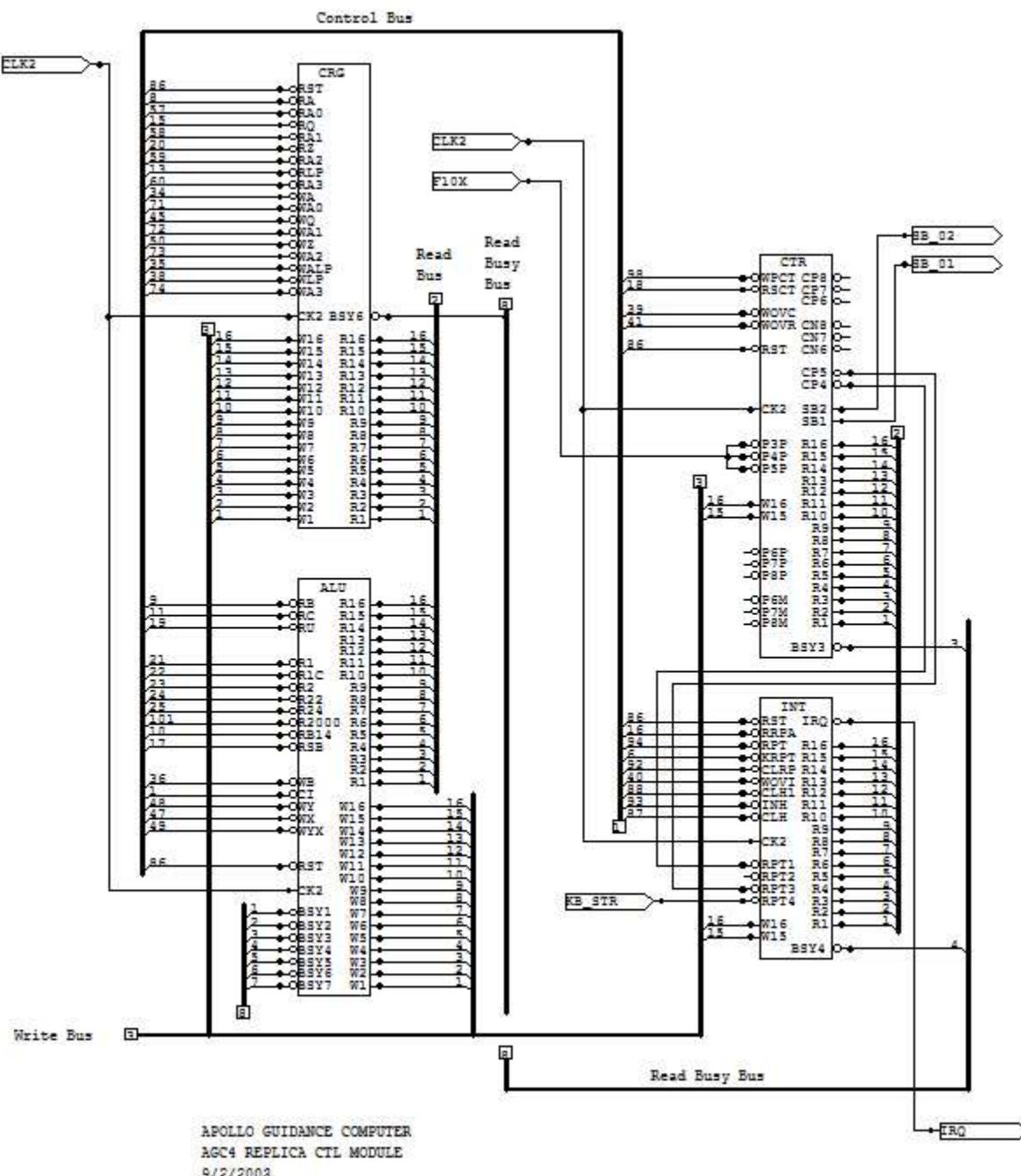
# PROC Internal Subsystem Interconnections


This diagram shows internal interconnections for the subsystems in the PROC module.



APOLLO GUIDANCE COMPUTER  
AGC4 REPLICA CTL MODULE  
9/2/2003
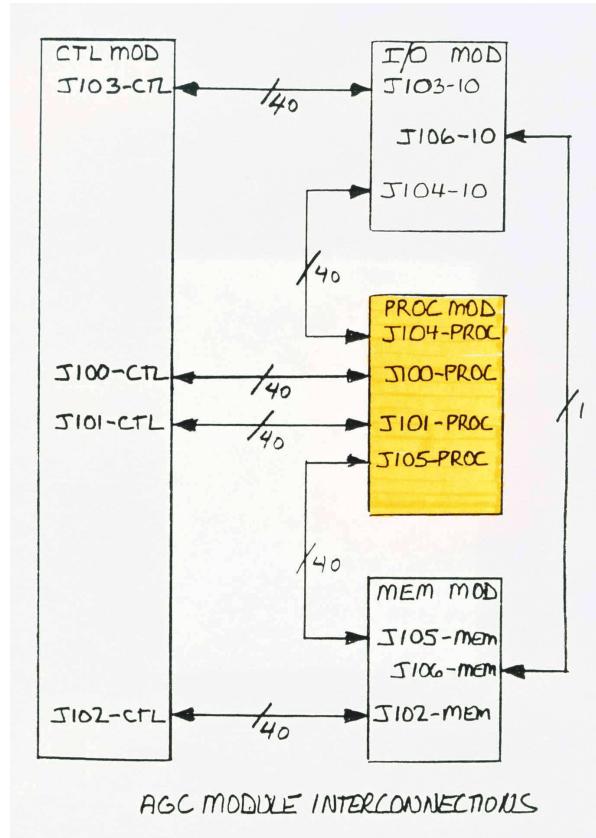
## PROC Module External Interfaces

The PROC module interfaces to the CTL, MEM, and IO modules through 40-pin IDE ribbon cables.




**J100-PROC: PROC-to-CTL I/F**

J100 is a 40-pin IDE cable that connects the PROC module to the CTL module.

*INPUTS (to PROC):*

| <u>PIN</u> | <u>signal</u> | <u>full name</u>        | <u>state definition</u>         |
|------------|---------------|-------------------------|---------------------------------|
| 1          | WA3           | WRITE ADDR 3 (74)       | 0=Write reg at address 3 (LP)   |
| 2          | WA2           | WRITE ADDR 2 (73)       | 0=Write reg at address 2 (Z)    |
| 3          | WA1           | WRITE ADDR 1 (72)       | 0=Write reg at address 1 (Q)    |
| 4          | WA0           | WRITE ADDR 0 (71)       | 0=Write reg at address 0 (A)    |
| 5          | RA3           | READ ADDR 3 (60)        | 0=Read reg at address 3 (LP)    |
| 6          | RA2           | READ ADDR 2 (59)        | 0=Read reg at address 2 (Z)     |
| 7          | RA1           | READ ADDR 1 (58)        | 0=Read reg at address 1 (Q)     |
| 8          | RA0           | READ ADDR 0 (57)        | 0=Read reg at address 0 (A)     |
| 9          | WZ            | WRITE Z (50)            | 0=Write Z                       |
| 10         | WYx           | WRITE Y NO RESET (49)   | 0=Write Y (do not reset)        |
| 11         | WY            | WRITE Y (48)            | 0=Write Y                       |
| 12         | WX            | WRITE X (47)            | 0=Write X                       |
| 13         | WQ            | WRITE Q (45)            | 0=Write Q                       |
| 14         | WOVR          | WRITE OVF (41)          | 0=Write overflow                |
| 15         | WOVI          | WRITE OVF RUPT INH (40) | 0=Write overflow RUPT inhibit   |
| 16         | WOVC          | WRITE OVF CNTR (39)     | 0=Write overflow counter        |
| 17         | WLP           | WRITE LP (38)           | 0=Write LP                      |
| 18         | WB            | WRITE B (36)            | 0=Write B                       |
| 19         | WALP          | WRITE A/LP (35)         | 0=Write A and LP                |
| 20         | WA            | WRITE A (34)            | 0=Write A                       |
| 21         | F10X          | F10 SCALER ONESHOT      | 1=timed out (100.0 Hz)          |
| 23         | R24           | READ 24 (25)            | 0=Read 24                       |
| 24         | R22           | READ 22 (24)            | 0=Read 22                       |
| 25         | R2            | READ 2 (23)             | 0=Read 2                        |
| 26         | R1C           | READ 1 COMP (22)        | 0=Read 1 complimented           |
| 27         | R1            | READ 1 (21)             | 0=Read 1                        |
| 28         | RZ            | READ Z (20)             | 0=Read Z                        |
| 29         | RU            | READ U (19)             | 0=Read sum                      |
| 30         | RSCT          | READ CNTR ADDR (18)     | 0=Read selected counter address |
| 31         | RSB           | READ SIGN (17)          | 0=Read sign bit                 |
| 32         | RRPA          | READ RUPT ADDR (16)     | 0=Read RUPT address             |
| 33         | RQ            | READ Q (15)             | 0=Read Q                        |
| 34         | RLP           | READ LP (13)            | 0=Read LP                       |
| 35         | RC            | READ C (11)             | 0=Read C                        |
| 36         | RB14          | READ BIT 14 (10)        | 0=Read bit 14                   |
| 37         | RB            | READ B (9)              | 0=Read B                        |
| 38         | RA            | READ A (8)              | 0=Read A                        |
| 39         | KRPT          | KNOCK DOWN RUPT (6)     | 0=Knock down Rupt priority      |
| 40         | CI            | SET CARRY IN (1)        | 0=Carry in                      |

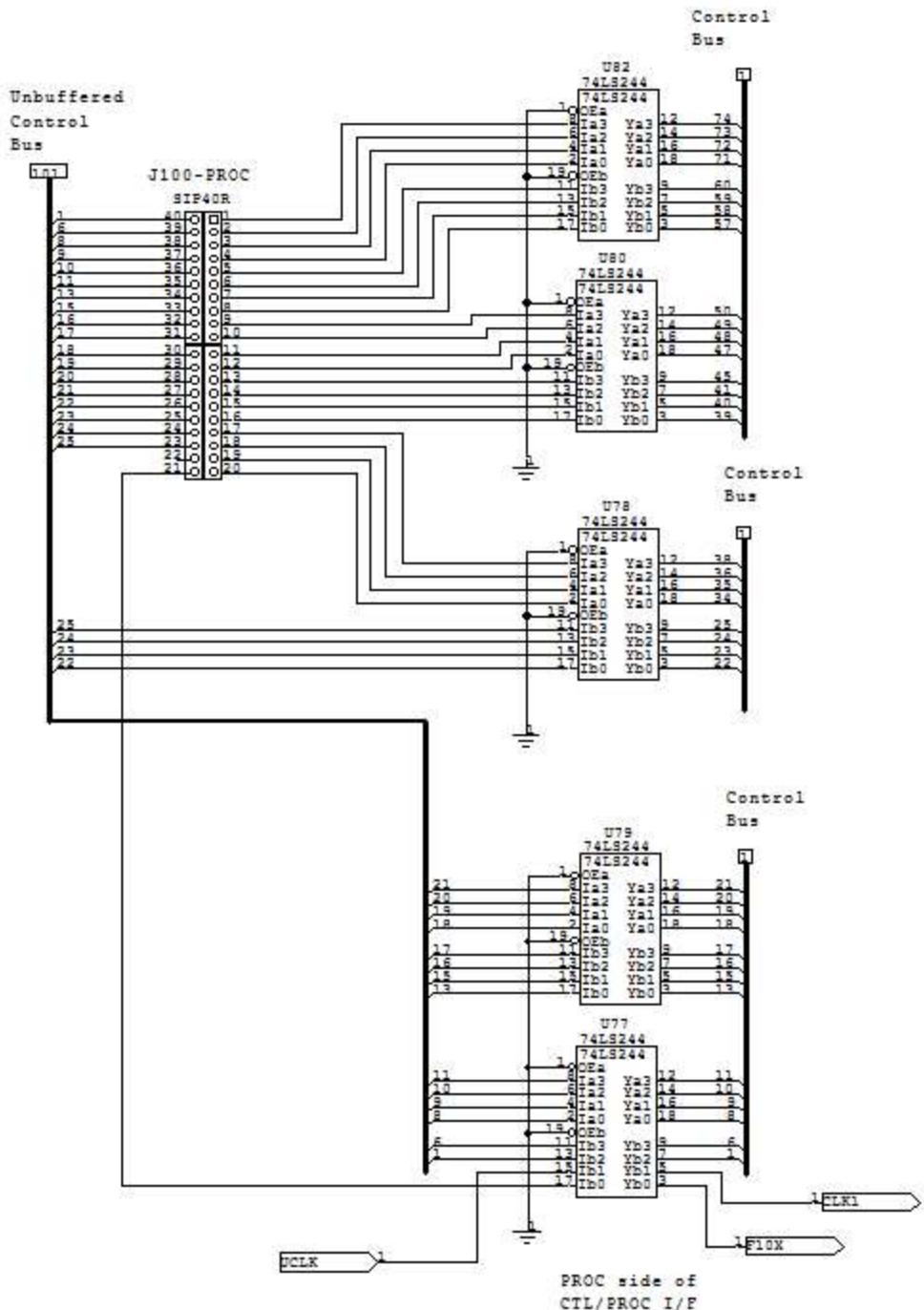

**J101-PROC: PROC-to-CTL I/F**


J101 is a 40-pin IDE cable that connects the PROC module to the CTL module.

*INPUTS (to PROC):*

| <u>PIN</u> | <u>signal</u> | <u>full name</u>   | <u>state definition</u>                   |
|------------|---------------|--------------------|---|
| 1          | R2000         | READ 2000 (101)    | 0=Read 2000                               |
| 2          | WPCTR         | WRITE PCTR (98)    | 0=Write PCTR (latch priority counter seq) |
| 3          | RPT           | READ RUPT (94)     | 0=Read RUPT opcode                        |
| 4          | INH           | SET INHINT (93)    | 0=Set INHINT                              |
| 5          | CLRP          | CLEAR RPCELL (92)  | 0=Clear RPCELL                            |
| 6          | CLINH1        | CLEAR INHINT1 (88) | 0=Clear INHINT1                           |
| 7          | CLINH         | CLEAR INHINT (87)  | 0=Clear INHINT                            |
| 8          | GENRST        | GENERAL RESET (86) | 0=General Reset                           |
| 19         | CLK1          | CLOCK1             | 1.024 MHz AGC clock 1 (normally low)      |
| 20         | CLK2          | CLOCK2             | 1.024 MHz AGC clock 2 (normally low)      |

*OUTPUTS (from PROC):*

| <u>PIN</u> | <u>signal</u> | <u>full name</u> | <u>state definition</u>         |
|------------|---------------|------------------|---------------------------------|
| 21         | SB_01         | SUB SEL 01       | SB_01 is LSB; SB_02 is MSB      |
| 22         | SB_02         | SUB SEL 02       | 00=no counter; 01=PINC; 10=MINC |
| 23         | IRQ           | INT RQST         | 0=interrupt requested.          |
| 25         | WB_01         | WRITE BUS 01     | (lsb)                           |
| 26         | WB_02         | WRITE BUS 02     |                                 |
| 27         | WB_03         | WRITE BUS 03     |                                 |
| 28         | WB_04         | WRITE BUS 04     |                                 |
| 29         | WB_05         | WRITE BUS 05     |                                 |
| 30         | WB_06         | WRITE BUS 06     |                                 |
| 31         | WB_07         | WRITE BUS 07     |                                 |
| 32         | WB_08         | WRITE BUS 08     |                                 |
| 33         | WB_09         | WRITE BUS 09     |                                 |
| 34         | WB_10         | WRITE BUS 10     |                                 |
| 35         | WB_11         | WRITE BUS 11     |                                 |
| 36         | WB_12         | WRITE BUS 12     |                                 |
| 37         | WB_13         | WRITE BUS 13     |                                 |
| 38         | WB_14         | WRITE BUS 14     |                                 |
| 39         | WB_15         | WRITE BUS 15     | US (overflow) bit               |
| 40         | WB_16         | WRITE BUS 16     | SG (sign) bit                   |

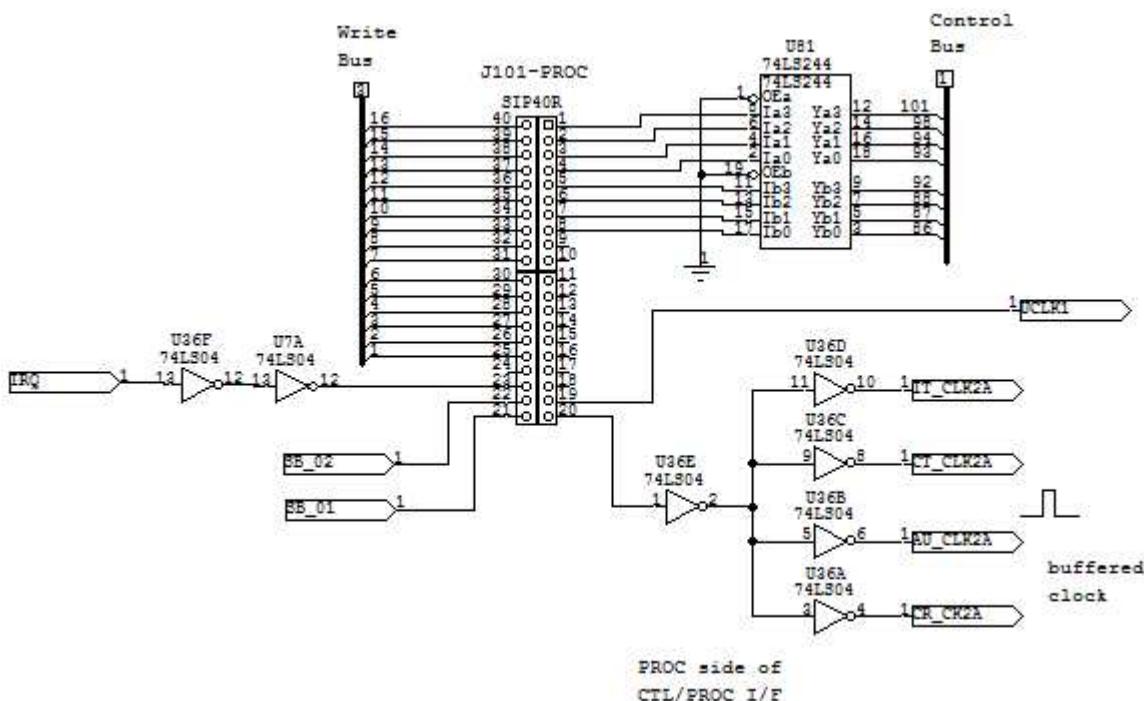

**J104-PROC: PROC-to-IO I/F**

J104 is a 40-pin IDE cable that connects the PROC module to the IO module.

*INPUTS (to PROC):*

| <u>PIN</u> | <u>signal</u> | <u>full name</u> | <u>state definition</u>  |
|------------|---------------|------------------|--|
| 40         | RB_01         | READ BUS 01      | (lsb)  |
| 39         | RB_02         | READ BUS 02      |  |
| 38         | RB_03         | READ BUS 03      |  |
| 37         | RB_04         | READ BUS 04      |  |
| 36         | RB_05         | READ BUS 05      |  |
| 35         | RB_06         | READ BUS 06      |  |
| 34         | RB_07         | READ BUS 07      |  |
| 33         | RB_08         | READ BUS 08      |  |
| 32         | RB_09         | READ BUS 09      |  |
| 31         | RB_10         | READ BUS 10      |  |
| 30         | RB_11         | READ BUS 11      |  |
| 29         | RB_12         | READ BUS 12      |  |
| 28         | RB_13         | READ BUS 13      |  |
| 27         | RB_14         | READ BUS 14      |  |
| 26         | RB_15         | READ BUS 15      | US (overflow) bit  |
| 25         | RB_16         | READ BUS 16      | SG (sign) bit  |
| 22         | BUSY2         | READ BUS BUSY    | 0=OUT register output to read bus  |
| 21         | BUSY1         | READ BUS BUSY    | 0=INP register output to read bus  |
| 20         | KB_STR        | KEY STROBE       | 1=key pressed strobe; to KEYRUPT. Key data is valid on the negative edge of KB_STR. Data is latched until the next keypress. |

*OUTPUTS (from PROC):*

| <u>PIN</u> | <u>signal</u> | <u>full name</u> | <u>state definition</u> |
|------------|---------------|------------------|-------------------------|
| 1          | WB_01         | WRITE BUS 01     | (lsb)                   |
| 2          | WB_02         | WRITE BUS 02     |                         |
| 3          | WB_03         | WRITE BUS 03     |                         |
| 4          | WB_04         | WRITE BUS 04     |                         |
| 5          | WB_05         | WRITE BUS 05     |                         |
| 6          | WB_06         | WRITE BUS 06     |                         |
| 7          | WB_07         | WRITE BUS 07     |                         |
| 8          | WB_08         | WRITE BUS 08     |                         |
| 9          | WB_09         | WRITE BUS 09     |                         |
| 10         | WB_10         | WRITE BUS 10     |                         |
| 11         | WB_11         | WRITE BUS 11     |                         |
| 12         | WB_12         | WRITE BUS 12     |                         |
| 13         | WB_13         | WRITE BUS 13     |                         |
| 14         | WB_14         | WRITE BUS 14     |                         |
| 15         | WB_15         | WRITE BUS 15     | US (overflow) bit       |
| 16         | WB_16         | WRITE BUS 16     | SG (sign) bit           |

**J105-PROC: PROC-to-MEM I/F**


J105 is a 40-pin IDE cable that connects the PROC module to the MEM module.

*INPUTS (to PROC):*

| <u>PIN</u> | <u>signal</u> | <u>full name</u> | <u>state definition</u>                 |
|------------|---------------|------------------|---|
| 40         | RB_01         | READ BUS 01      | (lsb)                                   |
| 39         | RB_02         | READ BUS 02      |   |
| 38         | RB_03         | READ BUS 03      |   |
| 37         | RB_04         | READ BUS 04      |   |
| 36         | RB_05         | READ BUS 05      |   |
| 35         | RB_06         | READ BUS 06      |   |
| 34         | RB_07         | READ BUS 07      |   |
| 33         | RB_08         | READ BUS 08      |   |
| 32         | RB_09         | READ BUS 09      |   |
| 31         | RB_10         | READ BUS 10      |   |
| 30         | RB_11         | READ BUS 11      |   |
| 29         | RB_12         | READ BUS 12      |   |
| 28         | RB_13         | READ BUS 13      |   |
| 27         | RB_14         | READ BUS 14      |   |
| 26         | RB_15         | READ BUS 15      | US (overflow) bit                       |
| 25         | RB_16         | READ BUS 16      | SG (sign) bit                           |
| 22<br>bus  | BUSY7         | READ BUS BUSY    | 0=BNK register output enabled to read   |
| 21         | BUSY5         | READ BUS BUSY    | 0=G register output enabled to read bus |

*OUTPUTS (from PROC):*

| <u>PIN</u> | <u>signal</u> | <u>full name</u> | <u>state definition</u> |
|------------|---------------|------------------|-------------------------|
| 1          | WB_01         | WRITE BUS 01     | (lsb)                   |
| 2          | WB_02         | WRITE BUS 02     |                         |
| 3          | WB_03         | WRITE BUS 03     |                         |
| 4          | WB_04         | WRITE BUS 04     |                         |
| 5          | WB_05         | WRITE BUS 05     |                         |
| 6          | WB_06         | WRITE BUS 06     |                         |
| 7          | WB_07         | WRITE BUS 07     |                         |
| 8          | WB_08         | WRITE BUS 08     |                         |
| 9          | WB_09         | WRITE BUS 09     |                         |
| 10         | WB_10         | WRITE BUS 10     |                         |
| 11         | WB_11         | WRITE BUS 11     |                         |
| 12         | WB_12         | WRITE BUS 12     |                         |
| 13         | WB_13         | WRITE BUS 13     |                         |
| 14         | WB_14         | WRITE BUS 14     |                         |
| 15         | WB_15         | WRITE BUS 15     | US (overflow) bit       |
| 16         | WB_16         | WRITE BUS 16     | SG (sign) bit           |

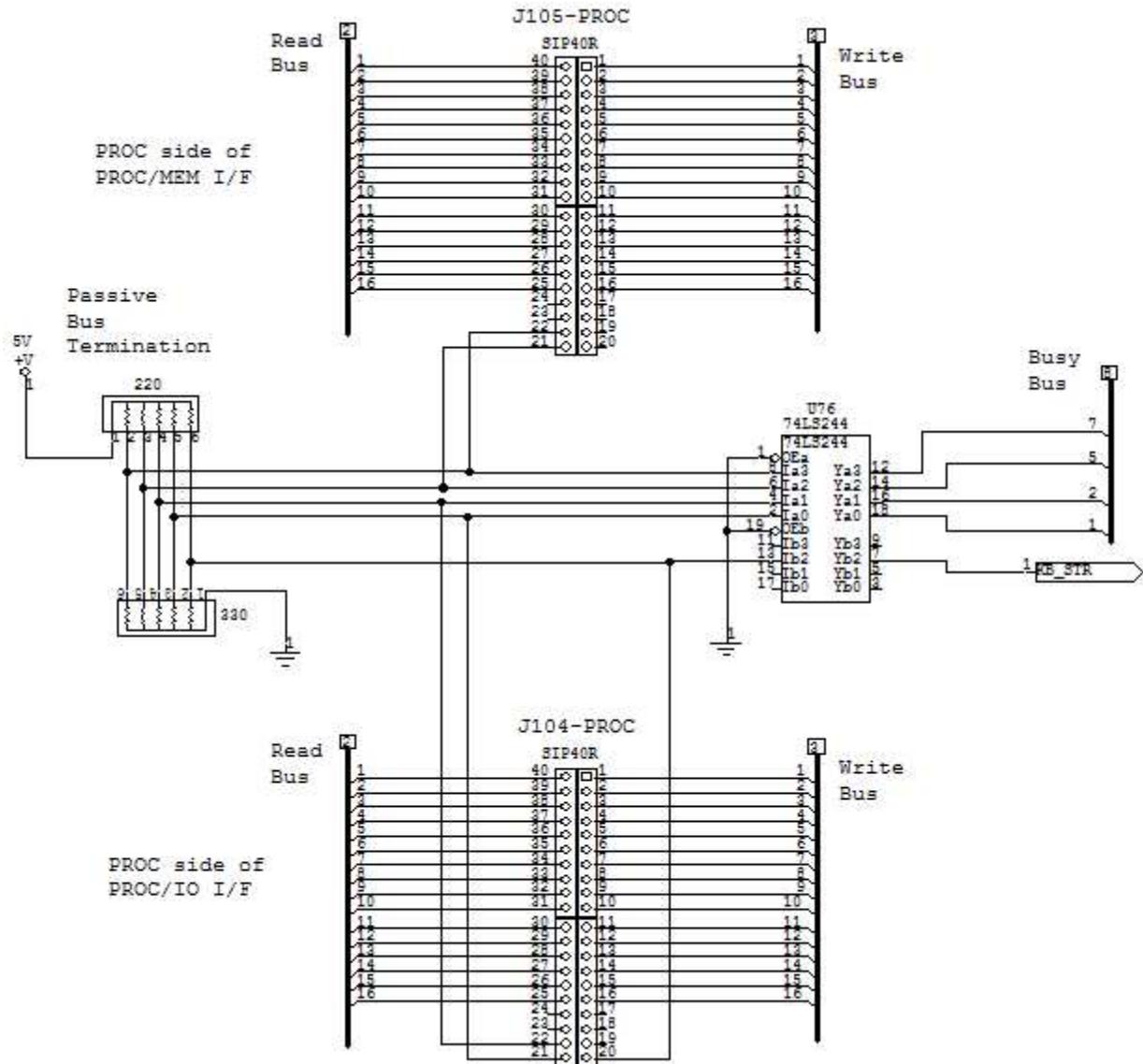

## PROC CONTROL PANEL PUSHBUTTONS



- |       |  |
|-------|--|
| RUPT1 | Set the RUPT1 flip-flop (FF). Simulates a TIME3 overflow. Triggers a T3RUPT.             |
| RUPT3 | Set the RUPT3 flip-flop (FF). Simulates a TIME4 overflow. Triggers a T4RUPT (DSRUPT).    |
| RUPT4 | Set the RUPT4 flip-flop (FF). Simulates a DSKY keypress. Triggers a KEYRUPT.             |
| TIME1 | Set the TIME1 flip-flop (FF). Increments the low-order word of the AGC real-time clock.  |
| TIME2 | Set the TIME2 flip-flop (FF). Increments the high-order word of the AGC real-time-clock. |
| TIME3 | Set the TIME3 flip-flop (FF). Increments the general purpose timer.                      |
| TIME4 | Set the TIME4 flip-flop (FF). Increments the display update timer.                       |


## **PROC CONTROL PANEL CONNECTIONS**

| <u>PIN</u> | <u>signal</u> | <u>state definition</u> |
|------------|---------------|-------------------------|
| 1          | RUPT1         | GND=set RUPT1 FF        |
| 2          | RUPT3         | GND=set RUPT3 FF        |
| 3          | RUPT4         | GND=set RUPT4 FF        |
| 4          | TIME1         | GND=set TIME1 FF        |
| 5          | TIME2         | GND=set TIME2 FF        |
| 6          | TIME3         | GND=set TIME3 FF        |
| 7          | TIME4         | GND=set TIME4 FF        |
| 8          | GND           |                         |

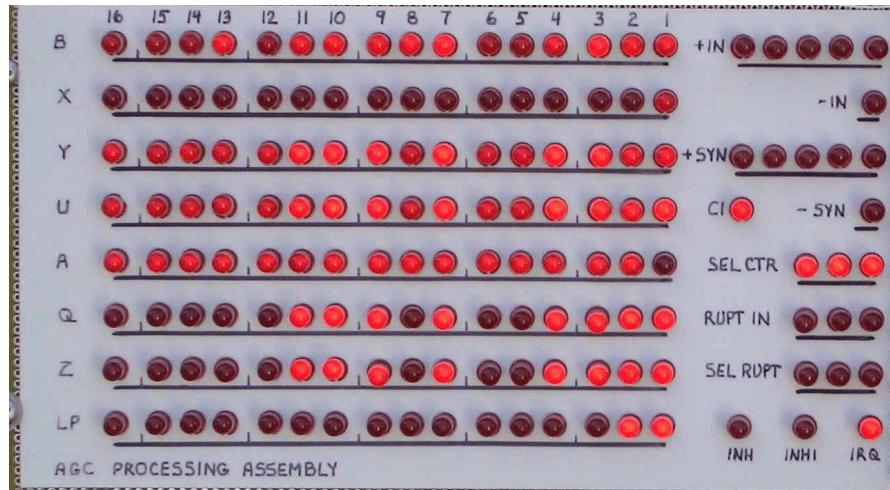
## PROC INDICATORS

The PROC module has a panel of indicator lamps (LEDs) to show the state of PROC registers and critical logic signals.


These indicator lamps show the current state of all registers and some additional, important logic signals produced by the PROC module. AGC numbers are represented in octal, so all register lamps are in groups of three. At the time the photo was taken the AGC was running the COLOSSUS 249 flight software load, executing Verb 16, Noun 36: a monitor verb which displays the AGC real time clock.




PROC ASSEMBLY  
INDICATORS #1



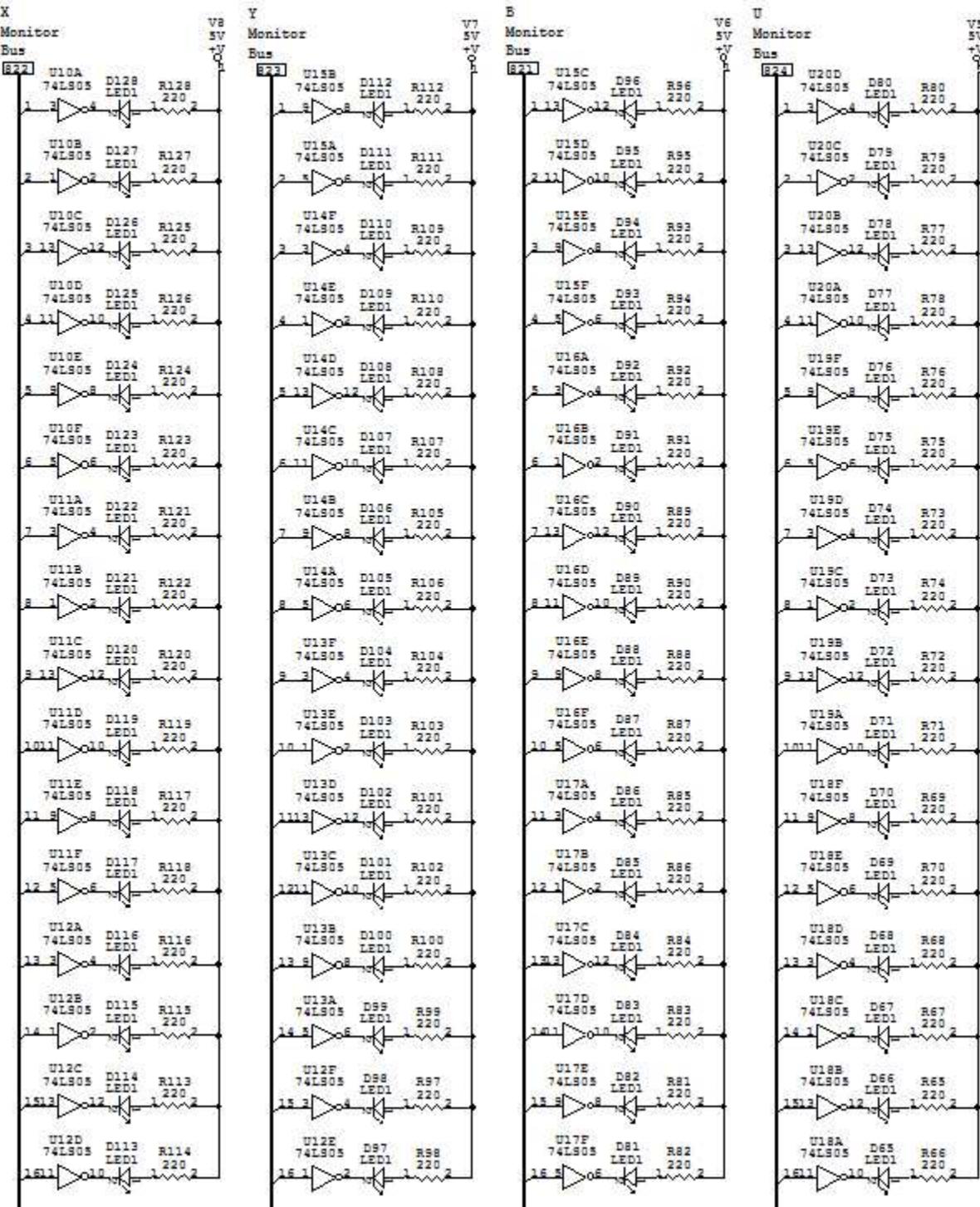


PROC ASSEMBLY  
INDICATORS #2

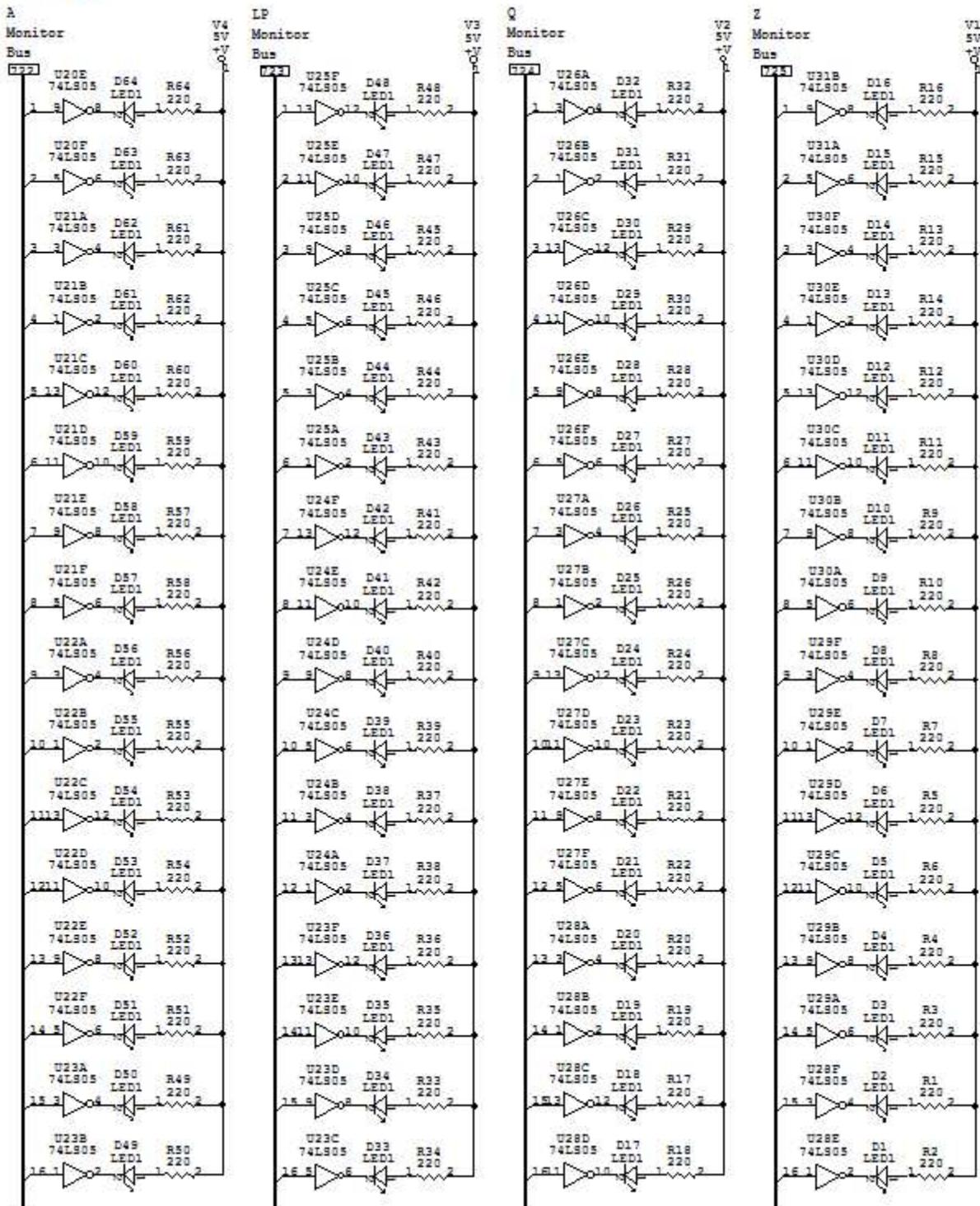

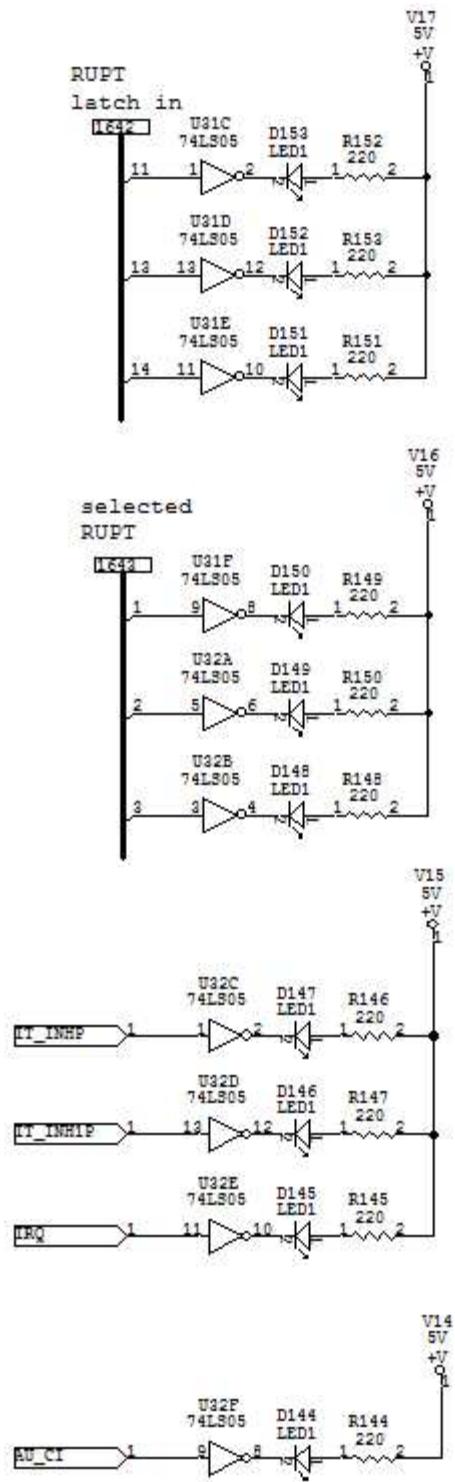


PROC ASSEMBLY  
INDICATORS #3

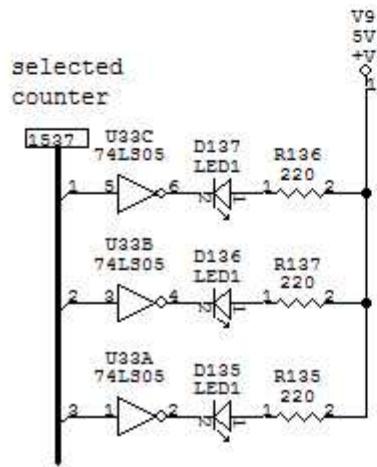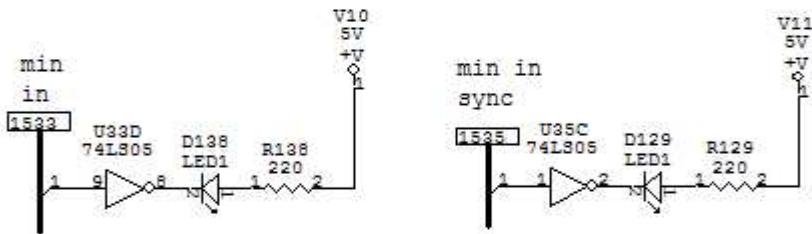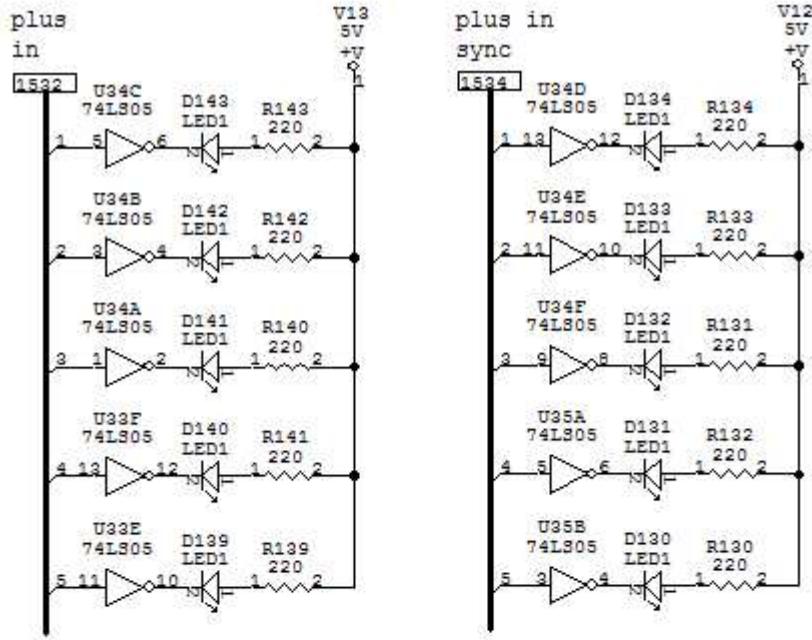

PROC ASSEMBLY  
INDICATORS #4
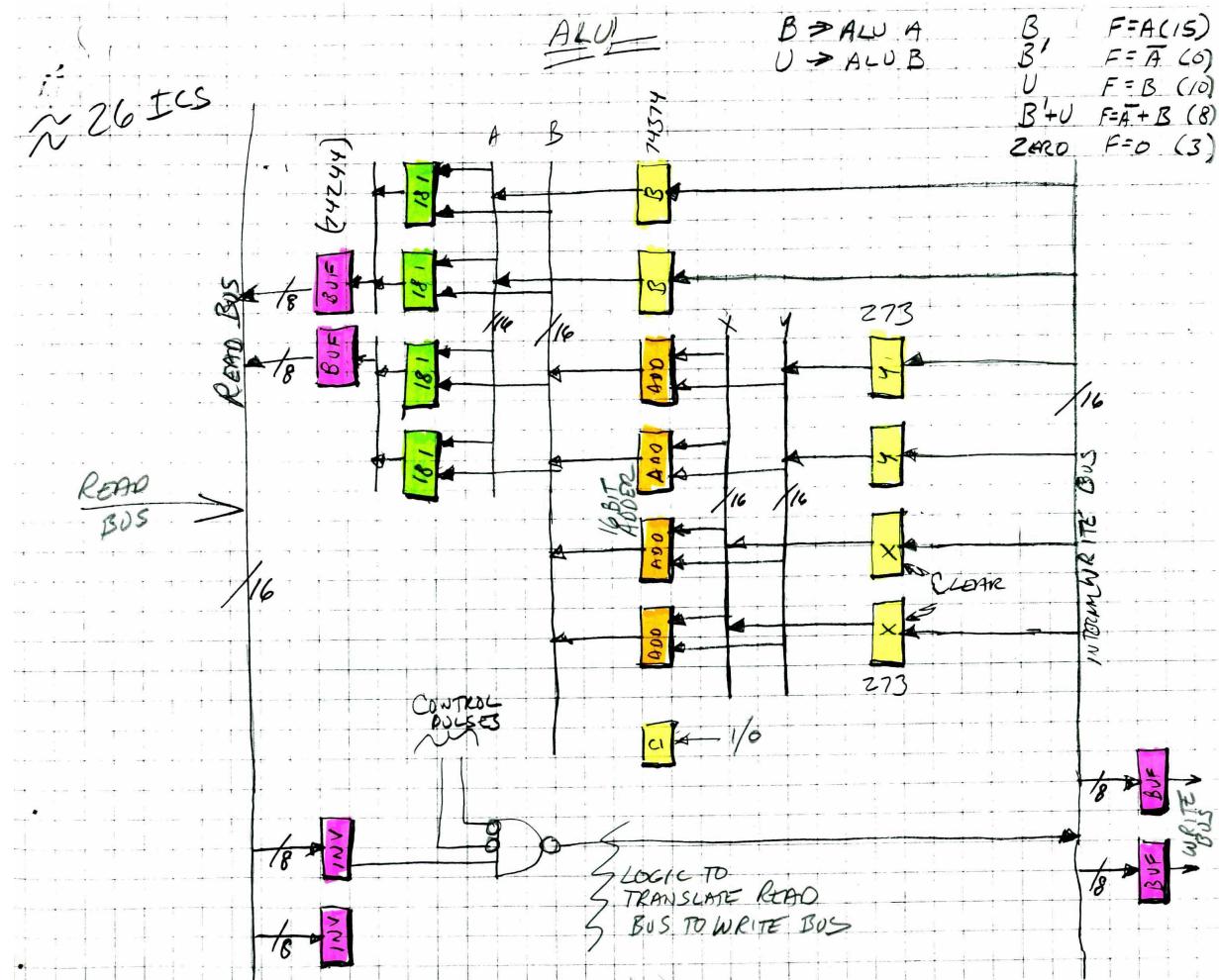
# ALU (Arithmetic Logic Unit)

My earliest architectural representation of the ALU logic is shown below:



The ALU contains the 16-bit ADDER (colored orange in the diagram) which performs 1's complement arithmetic, and increments the program counter (Z register). Each orange box is a 4-bit parallel adder; collectively, they add 16 bits. The ADDER uses the X, Y, and U registers:

- X: the 16-bit extension register (2 8-bit registers in yellow) that holds one of two inputs to the ADDER.
- Y: the 16-bit extension register (also in yellow) that holds the other input to the ADDER.
- U: the ADDER output (the 1's complement sum of the contents of registers X and Y). Outputs to the bus labeled "B" on the diagram.




The ALU also contains the B and C registers:

- B: a general-purpose buffer register (shown as 2 8-bit registers in yellow), also used to pre-fetch the next instruction. At the start of the next instruction sequence, the upper bits of B (containing the next op code) are copied to the SQ register (in CTL), and the lower bits (the address) are copied to the S register in (MEM). Output to the bus labeled "A" on the diagram.
- C: not a separate register, but the 1's complement of B.

The ALU contains logic (using 74LS181 ALU chips, shown in green) to do any of the following: select the B register; select the complement of the B register (the "C" register); select the U register; select the C register OR'ed with U, or select logical zero. Those logic functions, needed for AGC operation, are shown in the upper right corner of the diagram. The outputs of the 74LS181 selector are gated through a buffer to the read bus.

The original AGC could inclusive OR the outputs of any combination of registers onto the bus, but the control module only used this feature for the B/C and U registers. One of the uses involved the MASK instruction, which is a logical AND: DeMorgan's theorem was used to implement the equivalent of a logical AND by inverting operands through the C register, performing a logical OR through the bus, and then inverting the result.

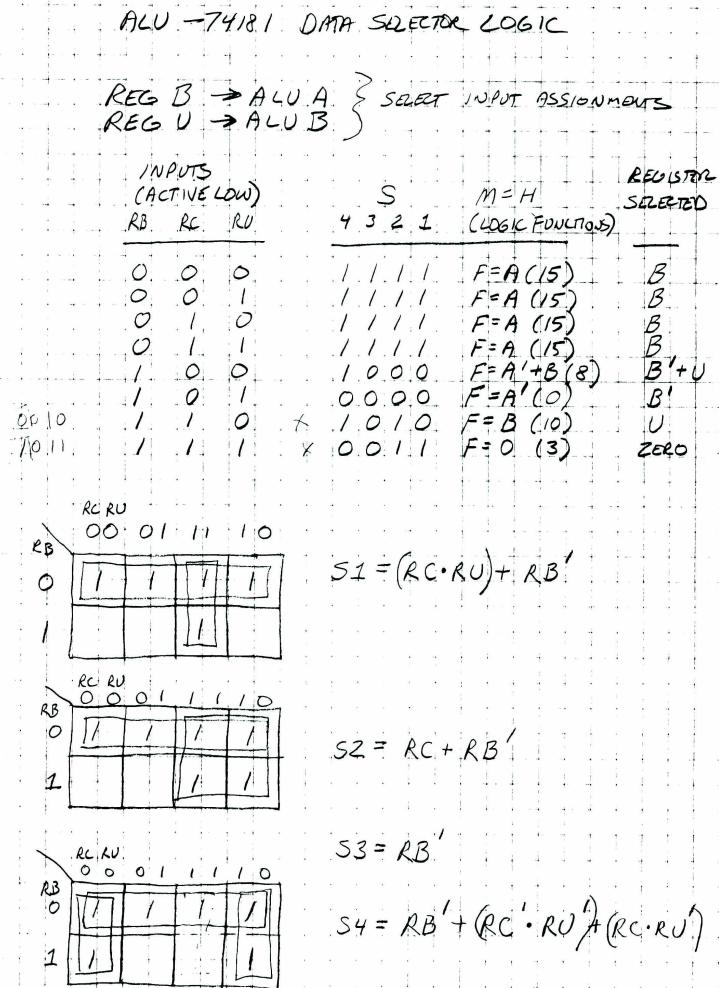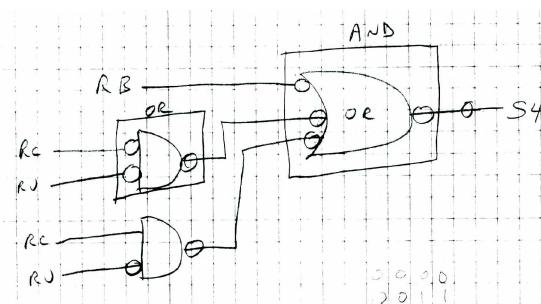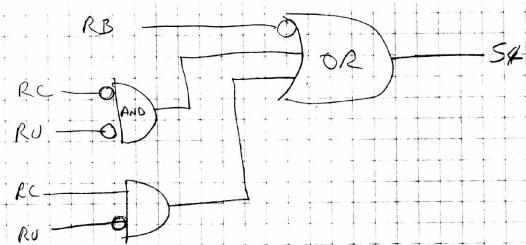The 74LS181 logic functions are gated to the read bus through the data selector logic, shown in the adjacent diagram.



The ALU also transfers data from the READ bus to the WRITE bus for register-to-register data moves: Data is output from the source register onto the READ bus, then transferred from the READ bus to the WRITE bus through the ALU, and finally loaded from the WRITE bus into the destination register.

The logic that translates the READ bus to the WRITE bus can also force the data lines of the WRITE bus to specific states to gate various arithmetic constants onto the bus. The accompanying diagram shows the control signal on the left (RB14, R1, etc) and to the right is the bit pattern that's OR'ed onto the bus when the signal is asserted. The default state of the read bus is logical zero, so if no other read signal is asserted, the number that appears on the bus is the constant; otherwise, it's the constant inclusive OR'ed with the contents of the READ bus.

The ALU contains READ bus control logic. Registers in the MEM module, the central registers in the PROC module, and the ALU all interface to the READ bus through tri-state buffers. These buffers are normally in the high-impedance state, but the control module (CTL) issues READ control signals to output the contents of specific registers to the READ bus at certain times. Only one register should be gated onto the READ bus at any given time.



When no READ control signals are asserted, the ALU gates its output onto the READ bus by default. When the control module gates a register onto the READ bus, a BUSY signal is sent to the ALU module, which causes the ALU to inhibit its output. Because of propagation delays, the ALU might continue to output to the READ bus for a brief time while another register is also gated to the bus. To prevent this, all output to the read bus is inhibited during CLK1. This gives the control signals, which transition on the leading edge of CLK1, enough setup time to resolve the conflict.

|       | <u>ALU</u> |    |    |    |    |    |    |   |   |   |   |   |   |   |   |   |
|-------|------------|----|----|----|----|----|----|---|---|---|---|---|---|---|---|---|
|       | 16         | 15 | 14 | 13 | 12 | 11 | 10 | 9 | 8 | 7 | 6 | 5 | 4 | 3 | 2 | 1 |
| RB14  | 0          | 0  | 1  | 0  | 0  | 0  | 0  | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| R1    | 0          | 0  | 0  | 0  | 0  | 0  | 0  | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| R1C   | 1          | 1  | 1  | 1  | 1  | 1  | 1  | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 |
| R2    | 0          | 0  | 0  | 0  | 0  | 0  | 0  | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| RSB   | 1          | 0  | 0  | 0  | 0  | 0  | 0  | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| R22   | 0          | 0  | 0  | 0  | 0  | 0  | 0  | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| R24   | 0          | 0  | 0  | 0  | 0  | 0  | 0  | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 |
| R2000 | 0          | 0  | 1  | 0  | 0  | 0  | 0  | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

→ 0 1 0 1 1 1 1 1 1 0 1 0 0 1 0 1 1  
OR'ed w/READ BUS


2-4 input OR

| CTL READ | Parity |
|----------|--------|
| 0 0 1    | 0      |
| 0 1 1    | 0      |
| 1 0 0    | 0      |
| 1 1 1    | 1      |

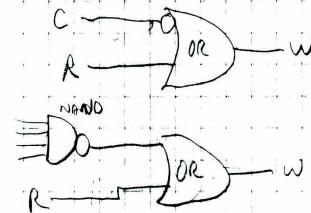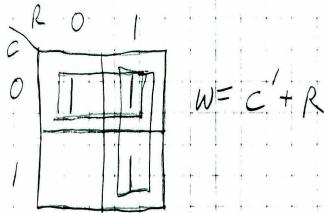

## ALU INPUTS:

| <u>I/F</u> | <u>signal</u> | <u>full name</u> | <u>state definition</u>                 |
|------------|---------------|------------------|---|
| CLK:       |               |                  |   |
|            | CLK1          | CLOCK 1          | 1=read bus setup; inhibit read bus out  |
|            | CLK2          | CLOCK 2          | data transfer occurs on falling edge    |
| CPM:       |               |                  |   |
|            | RB            | READ B           | 0=output B register to write bus        |
|            | RC            | READ C           | 0=output comp of reg B (C) to write bus |
|            | RU            | READ G           | 0=output U register to write bus        |
|            | R1            | READ OCTAL 1     | 0=incl OR 000001 w/write bus            |
|            | R1C           | READ OCTAL -1    | 0=incl OR 177776 w/write bus            |
|            | R2            | READ OCTAL 2     | 0=incl OR 000002 w/write bus            |
|            | R22           | READ OCTAL 22    | 0=incl OR 000022 w/write bus            |
|            | R24           | READ OCTAL 24    | 0=incl OR 000024 w/write bus            |
|            | R2000         | READ OCTAL 2000  | 0=incl OR 002000 w/write bus            |
|            | RB14          | READ BIT14       | 0=incl OR 020000 w/write bus            |
|            | RSB           | READ SIGN BIT    | 0=incl OR 100000 w/write bus            |
|            | WB            | WRITE B          | 0=write into B from write bus           |
|            | CI            | WRITE CI         | 0=set carry register to 1               |
|            | WY            | WRITE Y          | 0=write Y                               |
|            | WX            | WRITE X          | 0=write into X from write bus           |
|            | WYX           | WRITE Y          | 0=write into Y from write bus           |
| RBUS:      |               |                  |   |
|            | RB_01         | READ BUS 01      |   |
|            | ...           |                  |   |
|            | RB_14         | READ BUS 14      |   |
|            | RB_15         | READ BUS 15      | US (overflow) bit for read bus          |
|            | RB_16         | READ BUS 16      | SG (sign) bit for read bus              |
| INP:       | BUSY1         | READ BUS BUSY    | 0=valid data from INP on read bus       |
| OUT:       | BUSY2         | READ BUS BUSY    | 0=valid data from OUT on read bus       |
| CTR:       | BUSY3         | READ BUS BUSY    | 0=valid data from CTR on read bus       |
| INT:       | BUSY4         | READ BUS BUSY    | 0=valid data from INT on read bus       |
| MBF:       | BUSY5         | READ BUS BUSY    | 0=valid data from MBF on read bus       |
| CRG:       | BUSY6         | READ BUS BUSY    | 0=valid data from CRG on read bus       |
| ADR:       | BUSY7         | READ BUS BUSY    | 0=valid data from ADR on read bus       |

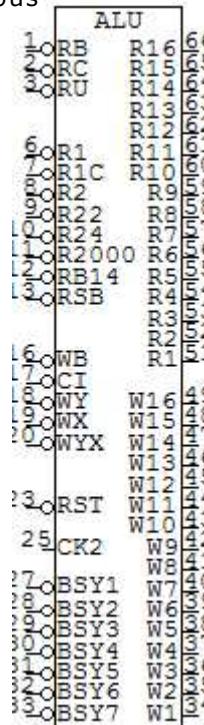



## MBF OUTPUTS:


| <u>I/F</u> | <u>signal</u> | <u>full name</u> | <u>state definition</u> |
|------------|---------------|------------------|-------------------------|
|------------|---------------|------------------|-------------------------|


WBUS:



|       |              |                                 |
|-------|--------------|---------------------------------|
| WB_01 | WRITE BUS 01 |                                 |
| ...   |              |                                 |
| WB_14 | WRITE BUS 14 |                                 |
| WB_15 | WRITE BUS 15 | US (overflow) bit for write bus |
| WB_16 | WRITE BUS 16 | SG (sign) bit for write bus     |

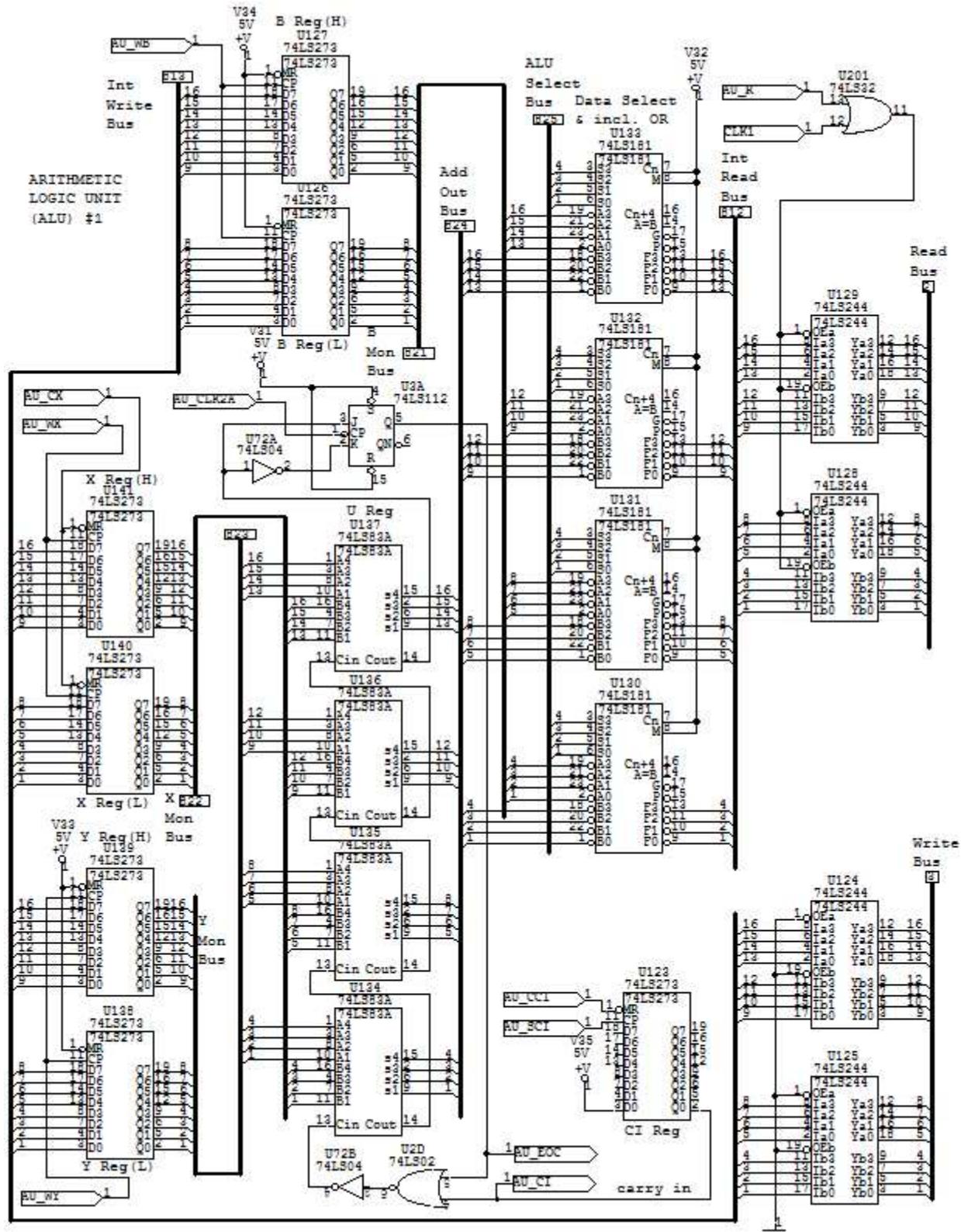

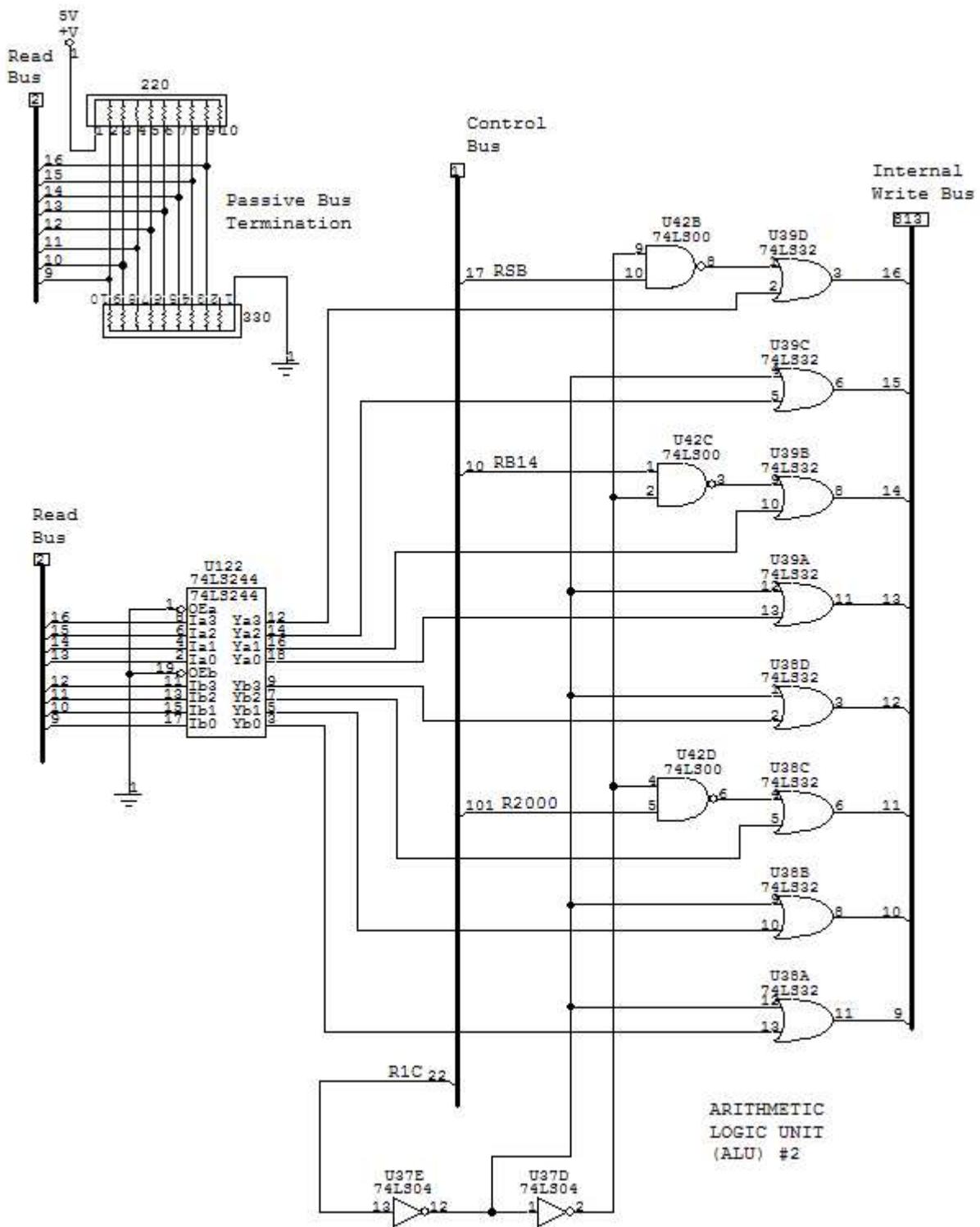

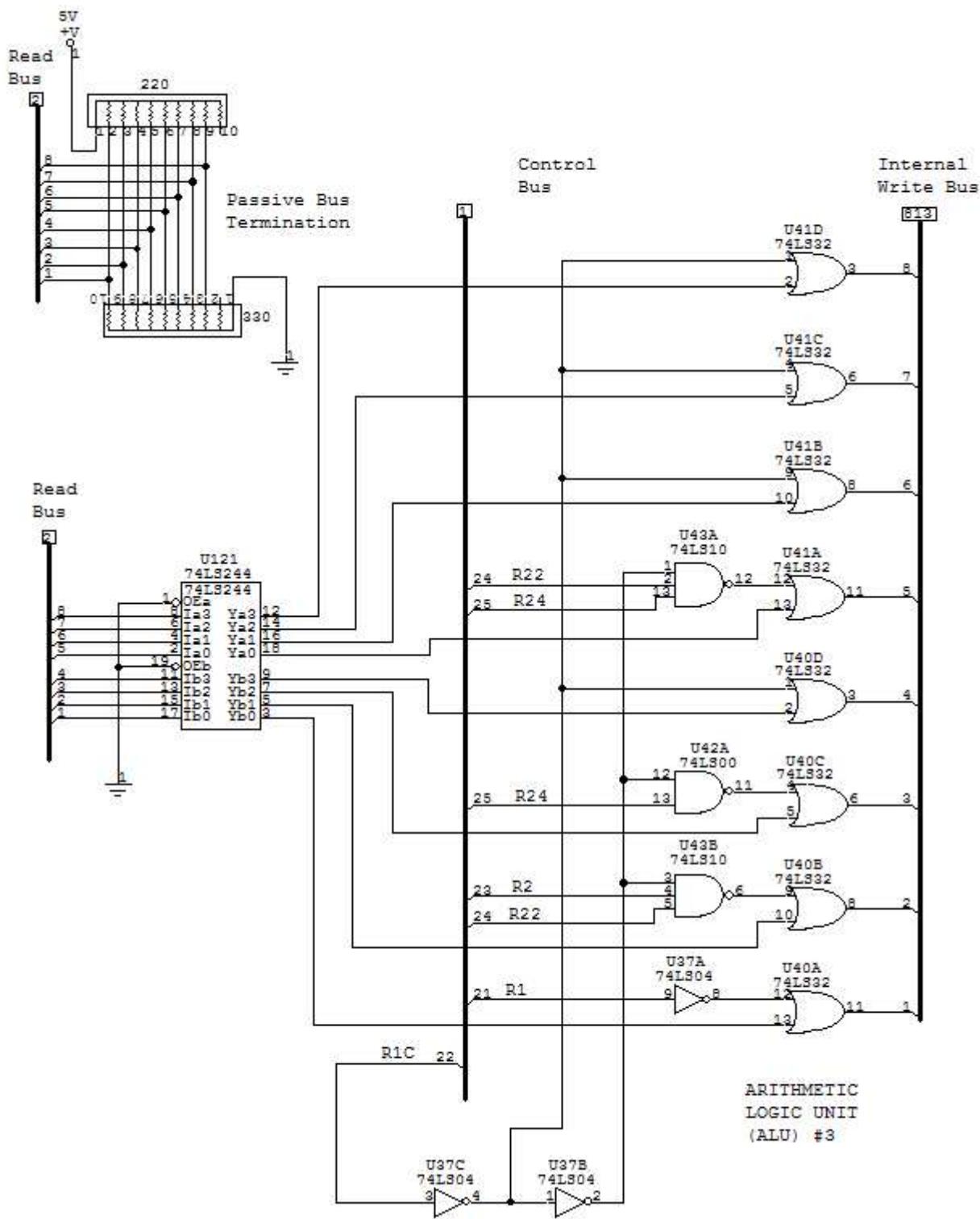

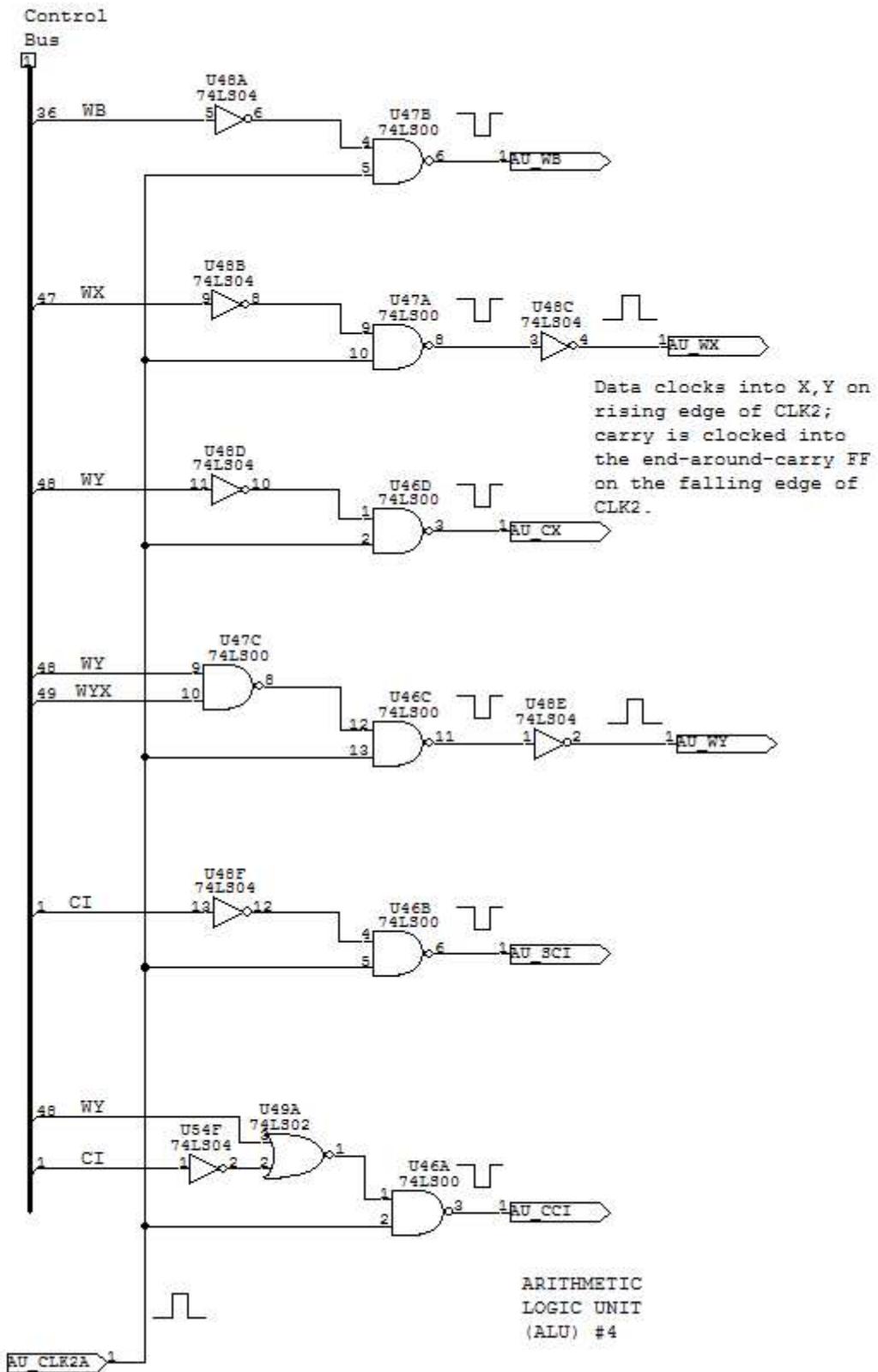

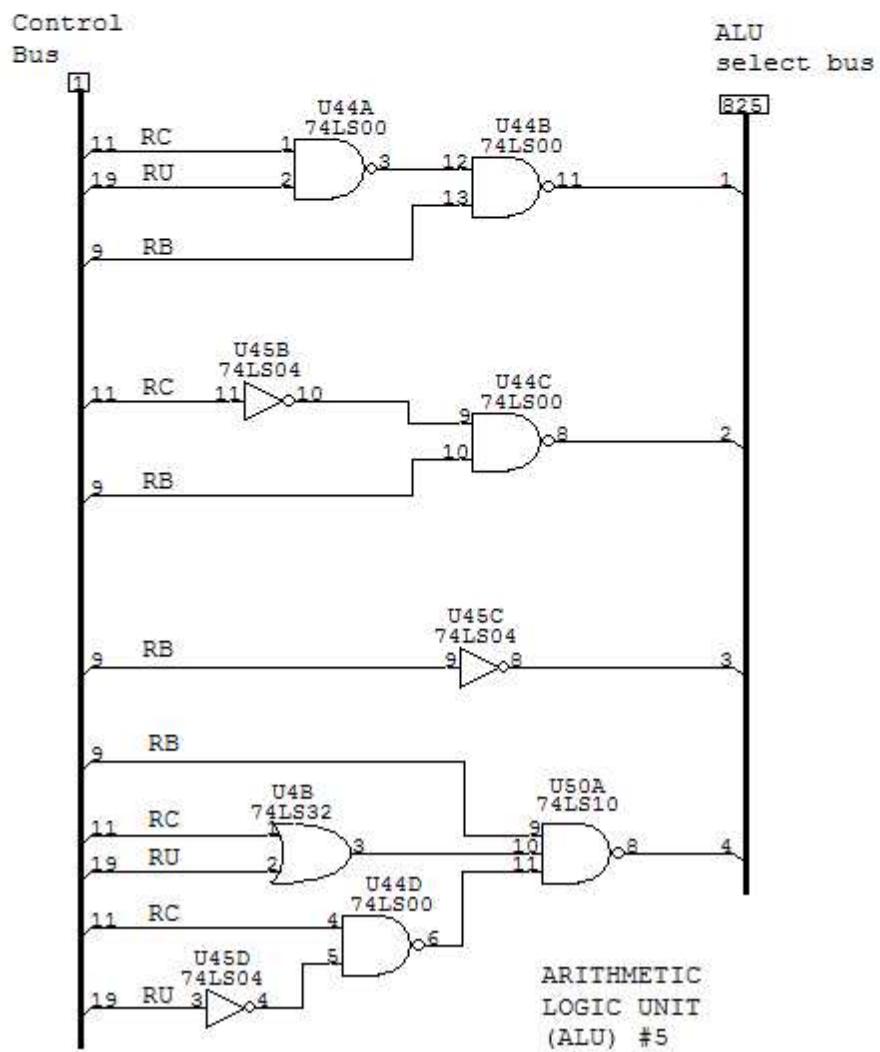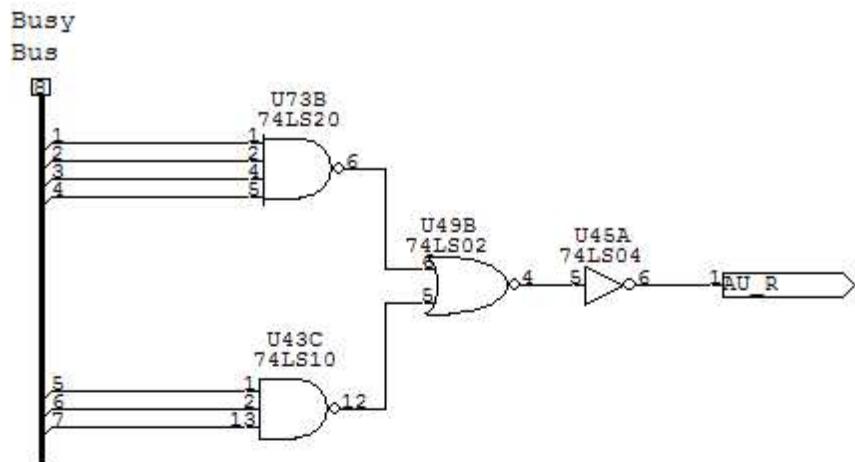

# CRG (Central Register)


The AGC has four 16-bit registers for general computational use. These are called the "central registers":

A: the 16-bit accumulator, used for general computation.

Z: the 16-bit program counter, which contains the address of the next instruction to be executed.

Q: the 16-bit register used to hold the remainder in the DV instruction, and to hold the return address after TC instructions.

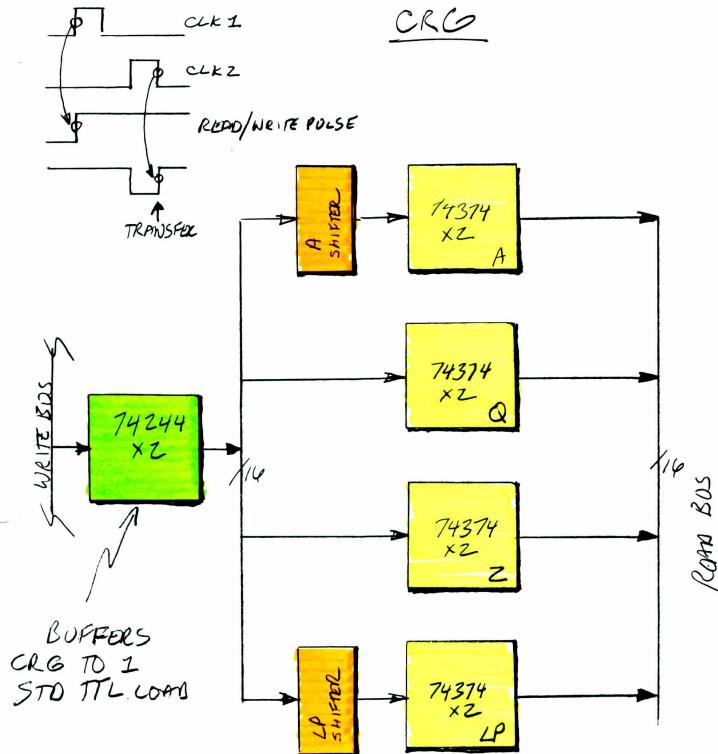LP: the 16-bit register used to hold the lower product after MP instructions.



## Register A and LP shifters

In addition to "normal" control pulses that write each line of the write bus into the corresponding bit of the registers, the A and LP registers have special write control pulses that shift bits:

The WALP control pulse bit-shifts into the A and LP register. The table below shows how the shifter works. The row of 16 comma-separated entries represent bits in the register. The leftmost position is the register MSB, rightmost position is the LSB. The entry shows the bit of the WRITE bus that's mapped onto that register bit by the shifter.

For the WALP pulse, bit 1 of the WRITE bus (B1) is written into bit 14 of the LP register. "BX" means leave that bit of the register alone (don't change it).

The same WALP pulse causes bit 2 of the WRITE bus (B2) to be written into the lowest bit of the A register, bit 3 of the WRITE bus (B3) to be written into the next bit, and so forth. "US" (uncorrected sign) is the overflow bit (bit 15) of the WRITE bus. "SG" is the 1's complement sign (bit 16) from the WRITE bus.

WALP for register LP:

BX, BX, B1, BX, BX

WALP for register A:

SG, SG, US, B14, B13, B12, B11, B10, B9, B8, B7, B6, B5, B4, B3, B2

Similarly, the WLP control pulse bit-shifts the WRITE bus into the LP register as follows (D0 on bit 14 of the LP register means force the bit to zero):

WLP

B1, B1, D0, B14, B13, B12, B11, B10, B9, B8, B7, B6, B5, B4, B3, B2

The logic design for handling bit 14 of the LP register, which takes control inputs from WALP, WLP, and WA3 is shown here. WA3 is identical to WLP.

Depending upon the WALP, WLP, or WA3 inputs, bit 14 of LP will either be set to B1 of the WRITE bus, or forced to zero.

| WA3 | WLP | B | C | D | B1 | B14          |
|-----|-----|---|---|---|----|--------------|
| 0   | 0   | 0 | 0 | 0 | X  | { ILLEGAL }  |
| 0   | 0   | 0 | 0 | 1 | X  |              |
| 0   | 0   | 1 | 0 | 0 | 0  |              |
| 0   | 0   | 1 | 1 | 1 | 0  |              |
| 0   | 1   | 0 | 0 | 0 | X  | { ILLEGAL }  |
| 0   | 1   | 0 | 0 | 1 | X  |              |
| 0   | 1   | 1 | 0 | 0 | 0  |              |
| 0   | 1   | 1 | 1 | 1 | 0  |              |
| 1   | 0   | 0 | 0 | 0 | X  | { ILLEGAL }  |
| 1   | 0   | 0 | 0 | 1 | X  |              |
| 1   | 0   | 1 | 0 | 0 | 0  |              |
| 1   | 0   | 1 | 1 | 1 | 0  |              |
| 1   | 1   | 0 | 0 | 0 | 0  |              |
| 1   | 1   | 0 | 0 | 1 | 1  |              |
| 1   | 1   | 1 | 0 | 0 | X  | { INACTIVE } |
| 1   | 1   | 1 | 1 | 1 | X  |              |

|    |   | CD | 00 | 01 | 11 | 10 |
|----|---|----|----|----|----|----|
| A  | B |    | X  | X  |    |    |
| 00 | X |    | X  |    |    |    |
| 01 | X |    | X  |    |    |    |
| 11 |   |    |    | 1  | X  | X  |
| 10 | X |    | X  |    |    |    |

$$B14 = C' \cdot D$$

LOGIC DESIGN FOR BIT 14 INPUT TO  
LP REGISTER

## CRG INPUTS:

| <u>I/F</u> | <u>signal</u> | <u>full name</u> | <u>state definition</u>   |
|------------|---------------|------------------|---|
| CLK:       |               |                  |   |
|            | CLK1          | CLOCK 1          |   |
|            | CLK2          | CLOCK 2          | 1=read bus setup; inhibit read bus output<br>data transfer occurs on falling edge |
| CPM:       |               |                  |   |
|            | RA            | READ A           | 0=output A to read bus  |
|            | RA0           | READ A           | 0=output A to read bus  |
|            | RQ            | READ Q           | 0=output Q to read bus  |
|            | RA1           | READ Q           | 0=output Q to read bus  |
|            | RZ            | READ Z           | 0=output Z to read bus  |
|            | RA2           | READ Z           | 0=output Z to read bus  |
|            | RLP           | READ LP          | 0=output LP to read bus   |
|            | RA3           | READ LP          | 0=output LP to read bus   |
|            | WA            | WRITE A          | 0=load A from write bus   |
|            | WA0           | WRITE A          | 0=load A from write bus   |
|            | WQ            | WRITE Q          | 0=load Q from write bus   |
|            | WA1           | WRITE Q          | 0=load Q from write bus   |
|            | WZ            | WRITE Z          | 0=load Z from write bus   |
|            | WA2           | WRITE Z          | 0=load Z from write bus   |
|            | WALP          | WRITE A,LP       | 0=load A,LP from write bus  |
|            | WLP           | WRITE LP         | 0=load LP from write bus  |
|            | GENRST        | GENERAL RESET    | 0=General Reset   |




## WBUS:

|       |              |                                 |
|-------|--------------|---------------------------------|
| WB_01 | WRITE BUS 01 |                                 |
| ...   |              |                                 |
| WB_14 | WRITE BUS 14 |                                 |
| WB_15 | WRITE BUS 15 | US (overflow) bit for write bus |
| WB_16 | WRITE BUS 16 | SG (sign) bit for write bus     |


## MBF OUTPUTS:

| <u>I/F</u> | <u>signal</u> | <u>full name</u> | <u>state definition</u>              |
|------------|---------------|------------------|--------------------------------------|
| RBUS:      |               |                  |                                      |
|            | RB_01         | READ BUS 01      |                                      |
|            | ...           |                  |                                      |
|            | RB_14         | READ BUS 14      |                                      |
|            | RB_15         | READ BUS 15      | US (overflow) bit for read/write bus |
|            | RB_16         | READ BUS 16      | SG (sign) bit for read/write bus     |
|            | BUSY          | READ BUS BUSY    | 0=output enabled to read bus         |

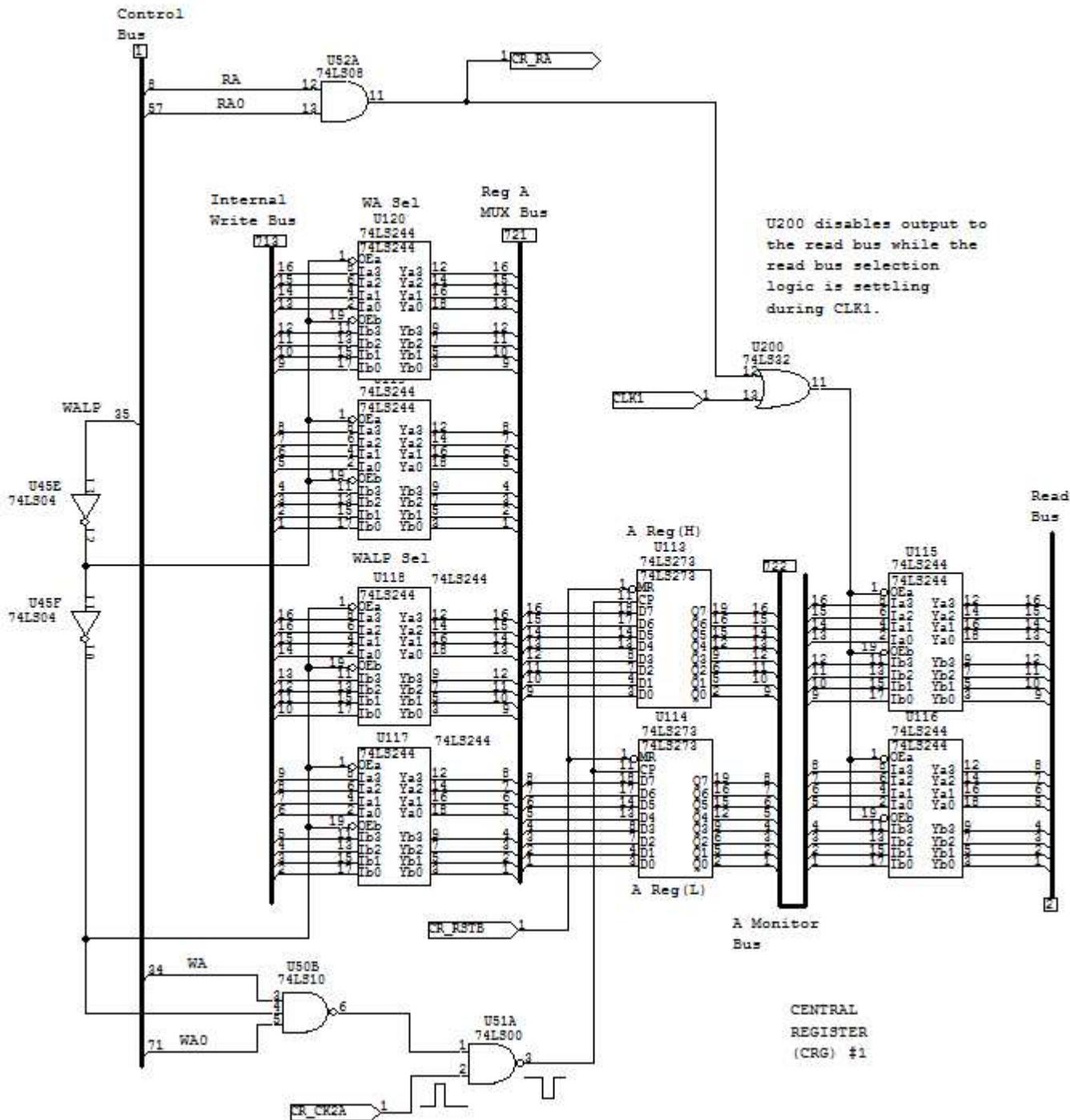




Control

Bus

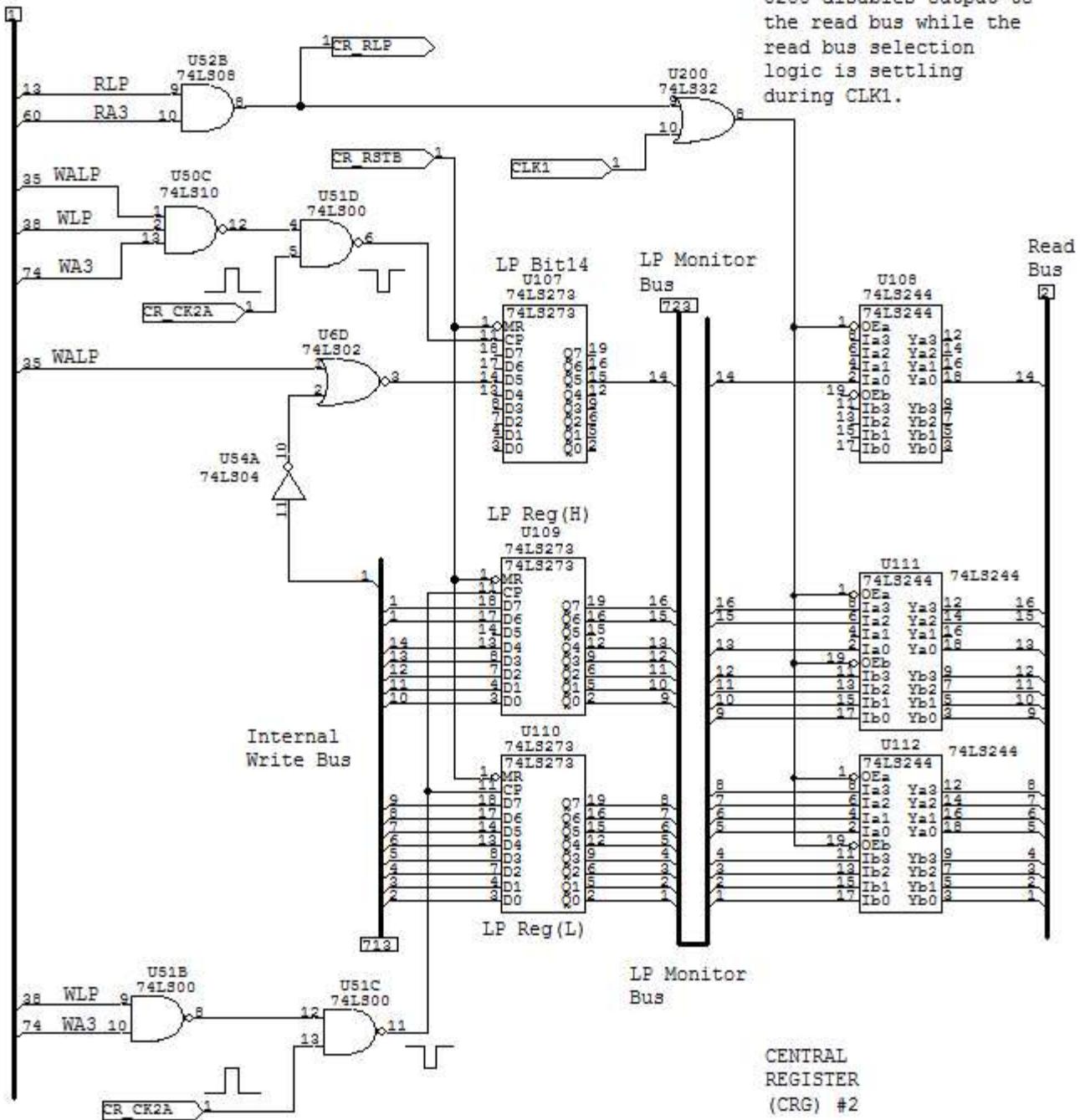

Control  
Bus

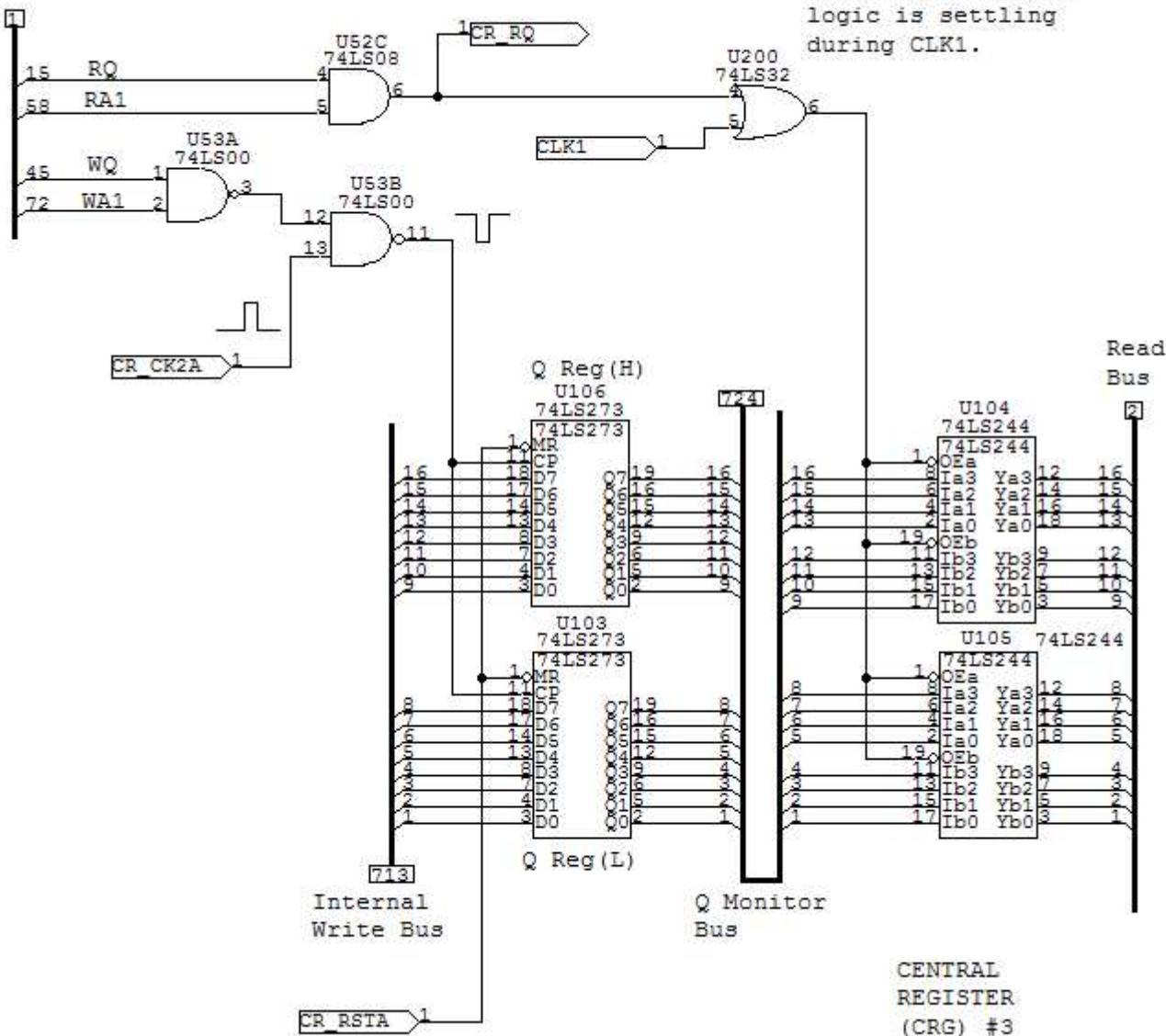

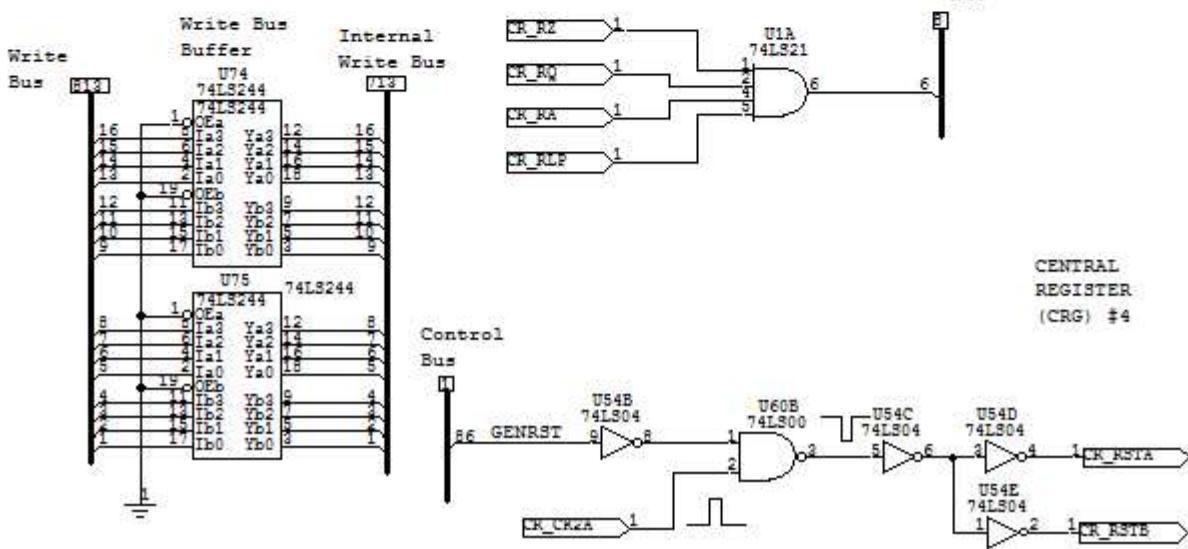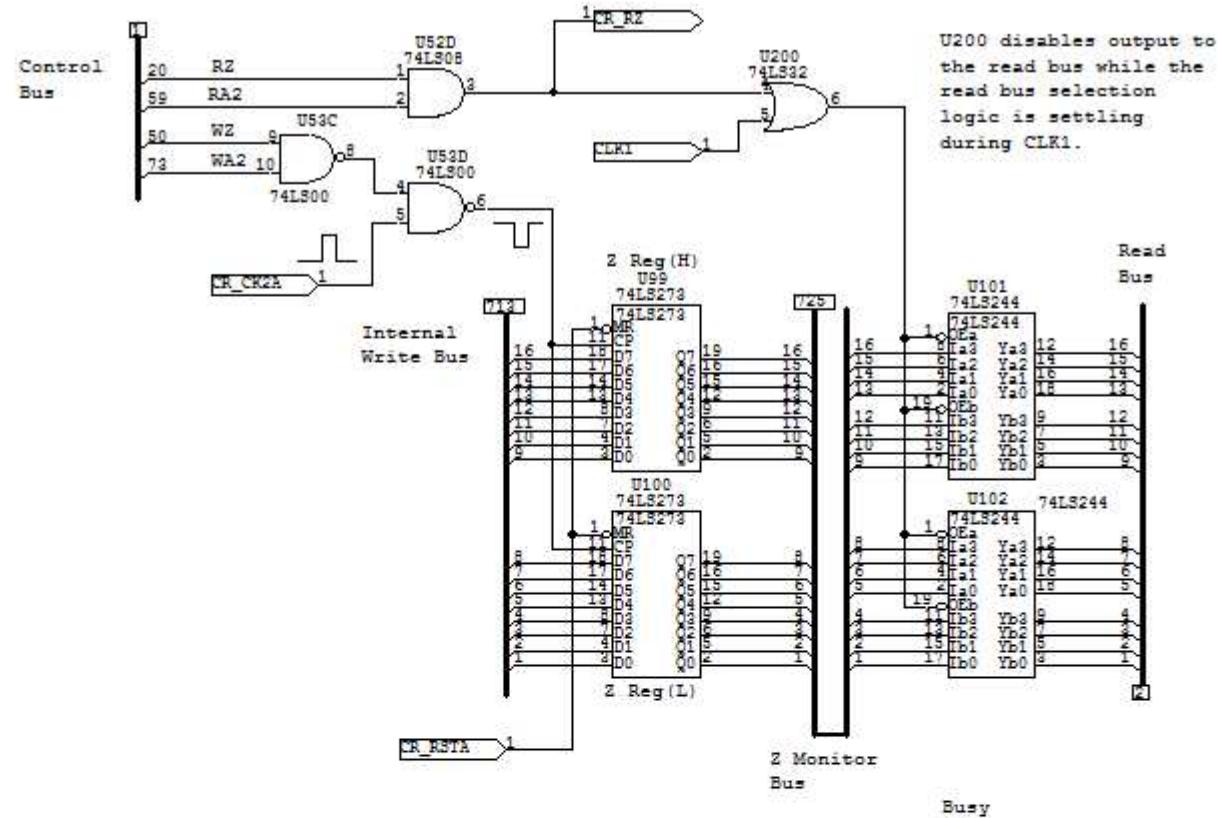

## **INT (Interrupt Priority)**

The original AGC had five vectored interrupts. This recreation implements the following 3:

- RUPT1      Also called T3RUPT because it's triggered by overflow of the TIME3 priority counter.
- RUPT3      Also called T4RUPT because it's triggered by overflow of the TIME4 priority counter. Because the interrupt is used by software to update the DSKY display at regular intervals, it's sometimes called DSRUPT.
- RUPT4      Triggered by a key press from the user's keyboard. Also called KEYRUPT.

The AGC software responds to each interrupt by temporarily suspending the current program, executing a short interrupt service routine, and then resuming the interrupted program.

## INT INPUTS:

| <u>I/F</u> | <u>signal</u> | <u>full name</u>     | <u>state definition</u>  |
|------------|---------------|----------------------|--|
| CLK:       |               |                      |  |
|            | CLK1          | CLOCK 1              |  |
|            | CLK2          | CLOCK 2              | 1=read bus setup; inhibit read bus out<br>data transfer occurs on falling edge |
| CPM:       |               |                      |  |
|            | GENRST        | GENERAL RESET        | 0=reset INT registers  |
|            | RRPA          | READ RUPT ADDRESS    | 0=output RPCELL address<br>(2004,2010,2014,2020,2024) to read bus              |
|            | RPT           | READ RUPT OPCODE     | 0=load RUPT opcode into RPCELL register  |
|            | KRPT          | KNOCK DOWN RUPT PRIO | 0=reset RUPT latch currently selected by<br>RPCELL register                    |
|            | CLRP          | CLEAR RPCELL         | 0=clear RPCELL register  |
|            | WOVI          | WRITE OVF RUPT INH   | 0=test overflow; if<br>overflow, inhibit interrupt<br>(set INHINT1)            |
|            | CLINH1        | CLEAR INHINT1        | 0=clear INHINT1 register   |
|            | INH           | SET INHINT           | 0=set INHINT register  |
|            | CLINH         | CLEAR INHINT         | 0=clear INHINT register  |
| WBUS:      |               |                      |  |
|            | WB_15         | WRITE BUS 15         | US (overflow) bit for write<br>bus   |
|            | WB_16         | WRITE BUS 16         | SG (sign) bit for write bus  |

| INT |       |                      |
|-----|-------|----------------------|
| 1   | ORST  | IRQ o <sup>40</sup>  |
| 2   | ORRPA |                      |
| 3   | ORPT  | R16 38               |
| 4   | OKRPT | R15 37               |
| 5   | OCLR  | R14 36               |
| 6   | OWOVI | R13 35               |
| 7   | OCLH1 | R12 34               |
| 8   | OINH  | R11 33               |
| 9   | OCLH  | R10 32               |
| 10  |       | R9 31                |
| 11  | CK2   | R8 30                |
| 12  |       | R7 29                |
| 13  | ORPT1 | R6 28                |
| 14  | ORPT2 | R5 27                |
| 15  | ORPT3 | R4 26                |
| 16  | ORPT4 | R3 25                |
| 17  | W16   | R2 24                |
| 18  |       | R1 23                |
| 19  | W15   |                      |
| 20  |       | BSY4 o <sup>21</sup> |

## CTR/KBD:

|       |             |  |
|-------|-------------|--|
| RUPT1 | INTERRUPT 1 | 0=trigger interrupt 1 (2004 octal; TIME3<br>overflow)                    |
| RUPT3 | INTERRUPT 3 | 0=trigger interrupt 3 (2014 octal; TIME4<br>overflow)                    |
| RUPT4 | INTERRUPT 4 | 0=trigger interrupt 4 (negative edge)<br>(2020 octal; keyboard activity) |

Note: interrupt cells above RUPT4 not implemented.


## INT OUTPUTS:


| <u>I/F</u> | <u>signal</u> | <u>full name</u> | <u>state definition</u>  |
|------------|---------------|------------------|--|
| SEQ:       |               |                  |  |
|            | IRQ           | INT RQST         | 0=interrupt requested. Active if all of the<br>following are true:<br>a) one or more RUPT FF's are set<br>b) interrupt is not currently being serviced |

c) interrupts are not inhibited

RBUS:

|       |               |                                      |
|-------|---------------|--------------------------------------|
| RB_01 | READ BUS 01   |                                      |
| ...   |               |                                      |
| RB_14 | READ BUS 14   |                                      |
| RB_15 | READ BUS 15   | US (overflow) bit for read/write bus |
| RB_16 | READ BUS 16   | SG (sign) bit for read/write bus     |
| BUSY  | READ BUS BUSY | 0=output enabled to read bus         |

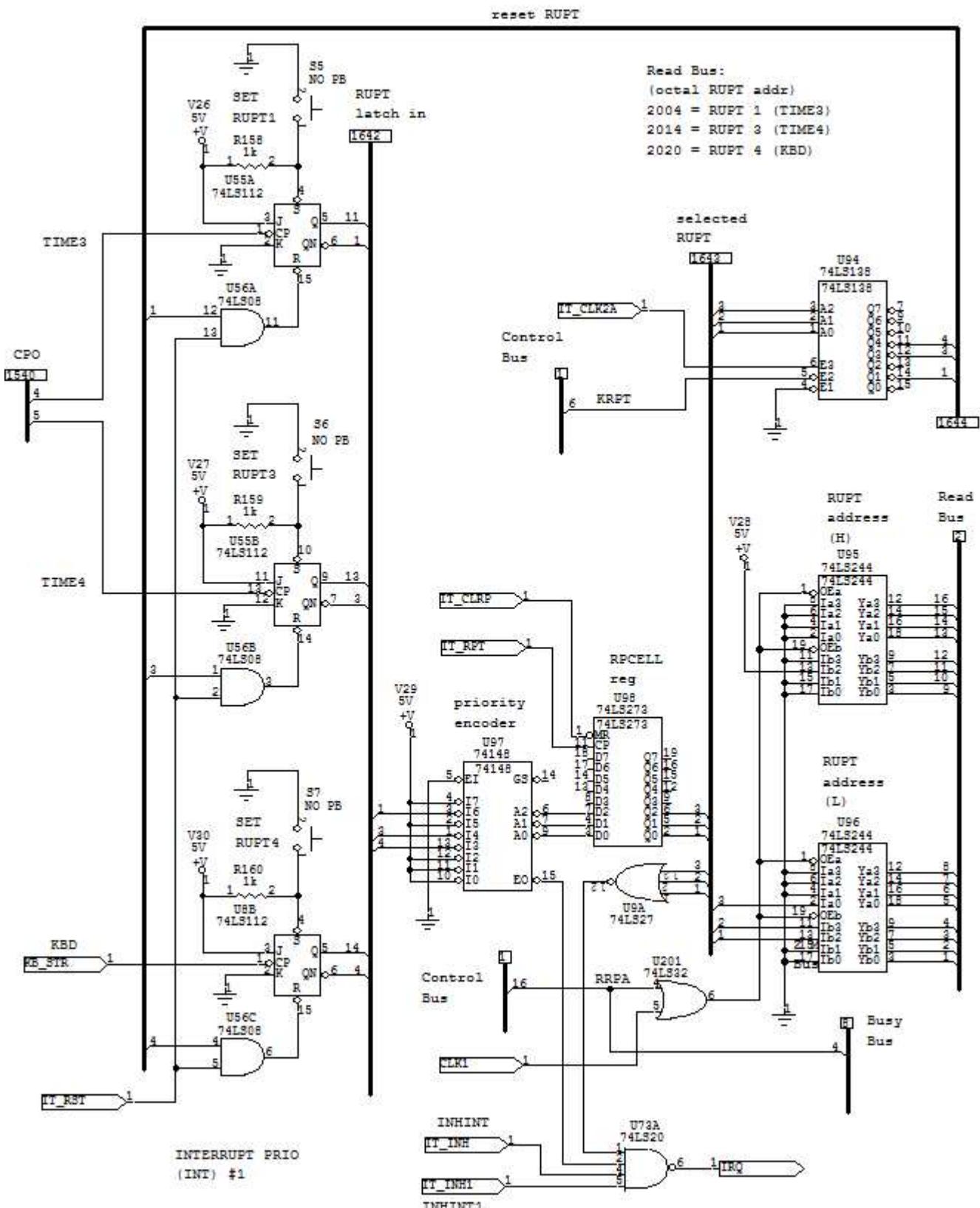

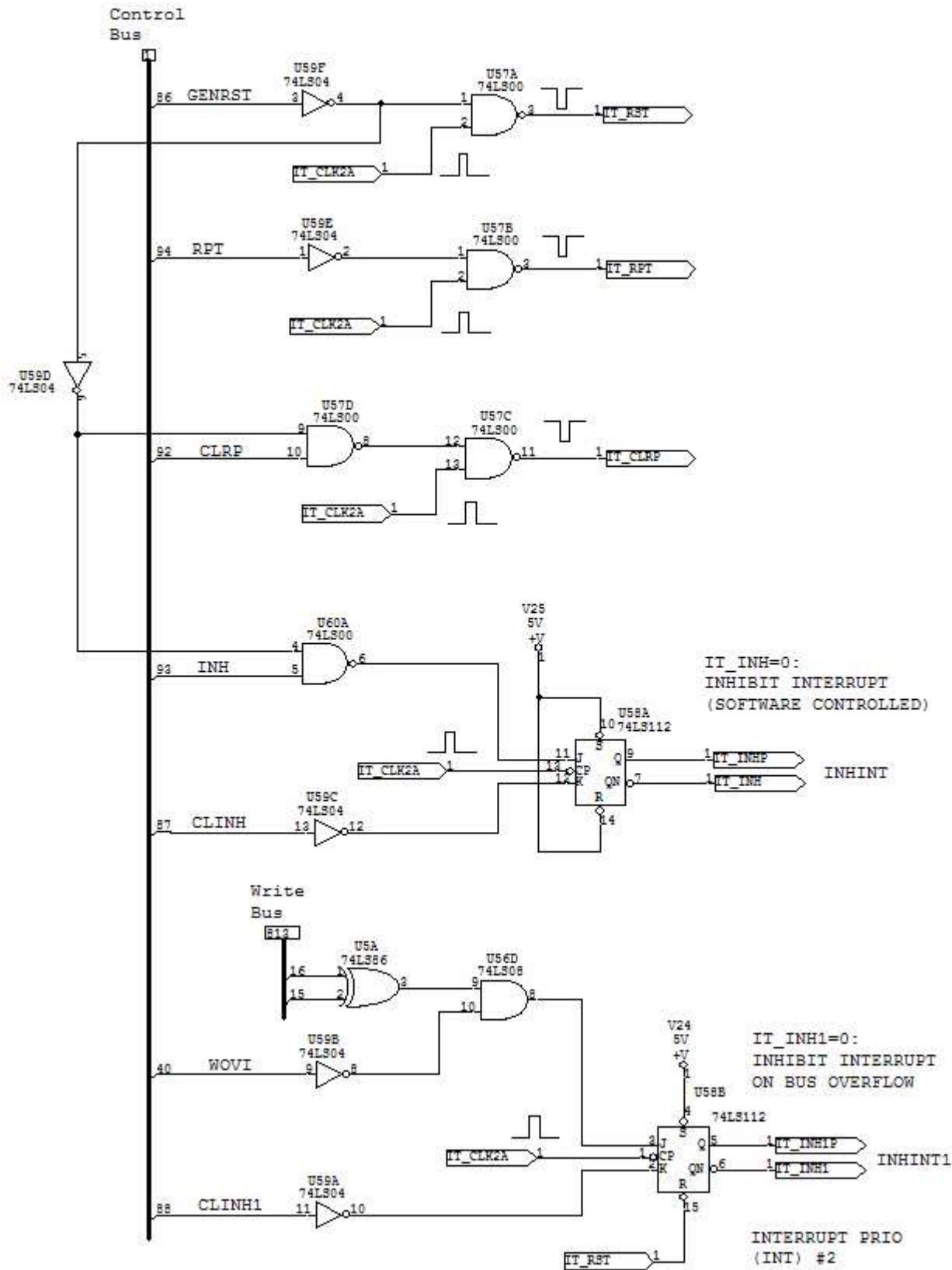

# CTR (Priority Counter)

The Block I AGC had 20 memory locations dedicated as up/down counters (involuntary counters). The counters would increment or decrement in response to external plus or minus logic signals. Increment (PINC) or decrement (MINC) was handled by one subsequence of microinstructions inserted between any two regular instruction subsequences when counter inputs occurred.

This replica implements 5 counters used by the AGC operating system and user interface:

| <u>Counter</u> | <u>Addr</u> | <u>Description</u>   |
|----------------|-------------|--|
| OVCTR          | 34          | An overflow counter incremented (PINC) or decremented (MINC) when overflow conditions occur during certain instructions.                               |
| TIME2          | 35          | The high-order bits of the AGC clock; incremented (PINC) by overflow of TIME1.   |
| TIME1          | 36          | The low-order bits of the AGC clock; incremented (PINC) by a 100Hz signal from the SCALER (SCL) in the control module (CTL).                           |
| TIME3          | 37          | A general purpose timer incremented by a 100Hz signal from the SCALER (SCL) in the control module (CTL).   |
| TIME4          | 40          | A special purpose timer used for software update of the DSKY display. Incremented by a 100Hz signal from the SCALER (SCL) in the control module (CTL). |

## INT/CTR interface


This chart shows how counter overflows are handled. F10 (from the scaler) increments TIME1, TIME3, and TIME4.

A positive overflow of TIME1 causes an increment of TIME2.

Positive overflow of TIME3 triggers a T3RUPT interrupt.

Positive overflow of TIME4 triggers a DSRUPT (T4RUPT) interrupt.

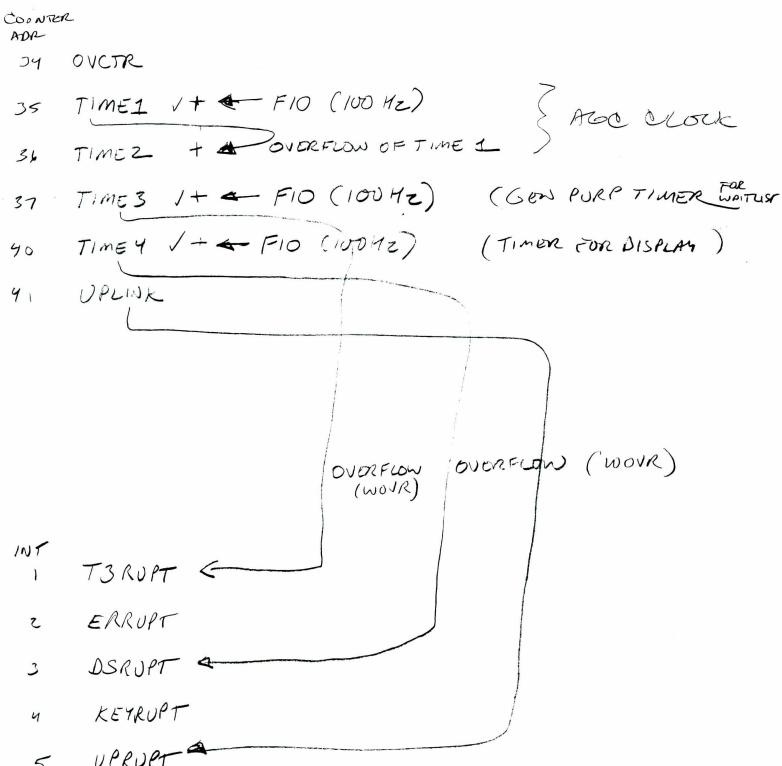The addresses of TIME1 and TIME2 are reversed for Block II. This chart shows the Block I order, but my replica used the Block II order for compatibility with the COLOSSUS flight software.



## **CTR Design Problem**

During unit testing, I uncovered a bug in my implementation of CTR: The plus inputs set the P-cell which eventually triggers a PINC subsequence and increments the counter. Minus inputs set the M-cell, which triggers a MINC subsequence and decrements the counter. Near-simultaneous plus and minus inputs should cancel out, producing no change in count.

As a consequence, the counter logic was designed so that, if the P- and M-cells are both set, no counter sequence (PINC or MINC) is selected. The problem is, the P- and M-cells are reset by WOVR, which only occurs in PINC or MINC. So, if both cells are set--and therefore, no subsequence is selected--WOVR is never issued, the cells never reset, and all counting activity is disabled for that counter.

Here are the options I developed fixing the design:

- a) Create a new subsequence similar to PINC or MINC that issues WOVR, but does not change the counter. Select this new subsequence when the P- and M-cells are simultaneously set.
- b) Allow the P- and M-cells to trigger PINC and MINC sequences, resulting in a net change of zero to the counter.
- c) Leave the design as-is, because the M-cell is only used for OVCTR in my implementation, and therefore, the problem can never occur.

I choose option C to avoid redesign and re-unit-testing of CTR.

## CTR INPUTS:

| <u>I/F</u> | <u>signal</u> | <u>full name</u>   | <u>state definition</u>  |
|------------|---------------|--------------------|--|
| CLK:       |               |                    |  |
|            | CLK1          | CLOCK 1            |  |
|            | CLK2          | CLOCK 2            | 1=read bus setup; inhibit read bus out<br>data transfer occurs on falling edge |
| CPM:       |               |                    |  |
|            | GENRST        | GENERAL RESET      | 0=reset CTR registers  |
|            | WPCTR         | WRITE PSEQ         | 0=write sequence into PSEQ   |
|            | RSCT          | READ PCELL ADDRESS | 0=output PCELL address (034-043) to read bus                                   |
|            | WOVC          | WRITE OVRFLOW CNTR | 0=test overflow and inc/dec OVCTR  |
|            | WOVR          | WRITE OVERFLOW     | 0=clear selected PCELL and handle counter overflow (if any)                    |
| WBUS:      |               |                    |  |
|            | WB_15         | WRITE BUS 15       | US (overflow) bit for write bus  |
|            | WB_16         | WRITE BUS 16       | SG (sign) bit for write bus  |
| EXTERNAL:  |               |                    |  |
|            | P3P           | P3 CELL + COUNT    | 0=count up P3 counter (036 octal; TIME1)                                       |
|            | P4P           | P4 CELL + COUNT    | 0=count up P4 counter (037 octal; TIME3)                                       |
|            | P5P           | P5 CELL + COUNT    | 0=count up P5 counter (040 octal, TIME4)                                       |



Note: priority cells 6-20 not implemented.

## CTR OUTPUTS:

| <u>I/F</u>        | <u>signal</u> | <u>full name</u> | <u>state definition</u>  |
|-------------------|---------------|------------------|--|
| COUNTER OVERFLOW: |               |                  |  |
|                   | CPO_04        | P4 + OVERFLOW    | 0=P4 cell pos ovf (during WOVR)<br>note: TIME3 + overflow; connect to INT subsystem to trigger T3RUPT interrupt. |
|                   | CPO_05        | P5 + OVERFLOW    | 0=P5 cell pos ovf (during WOVR)  |


note: TIME4 + overflow; connect  
to INT subsystem to trigger T4RUPT  
(DSRUPT) interrupt.


SEQ:


|       |            |                                 |
|-------|------------|---------------------------------|
| SB_01 | SUB SEL 01 | SB_01 is LSB; SB_02 is MSB      |
| SB_02 | SUB SEL 02 | 00=no counter; 01=PINC; 10=MINC |


RBUS:

|       |               |                                      |
|-------|---------------|--------------------------------------|
| RB_01 | READ BUS 01   |                                      |
| ...   |               |                                      |
| RB_14 | READ BUS 14   | US (overflow) bit for read/write bus |
| RB_15 | READ BUS 15   | SG (sign) bit for read/write bus     |
| RB_16 | READ BUS 16   |                                      |
| BUSY  | READ BUS BUSY | 0=output enabled to read bus         |

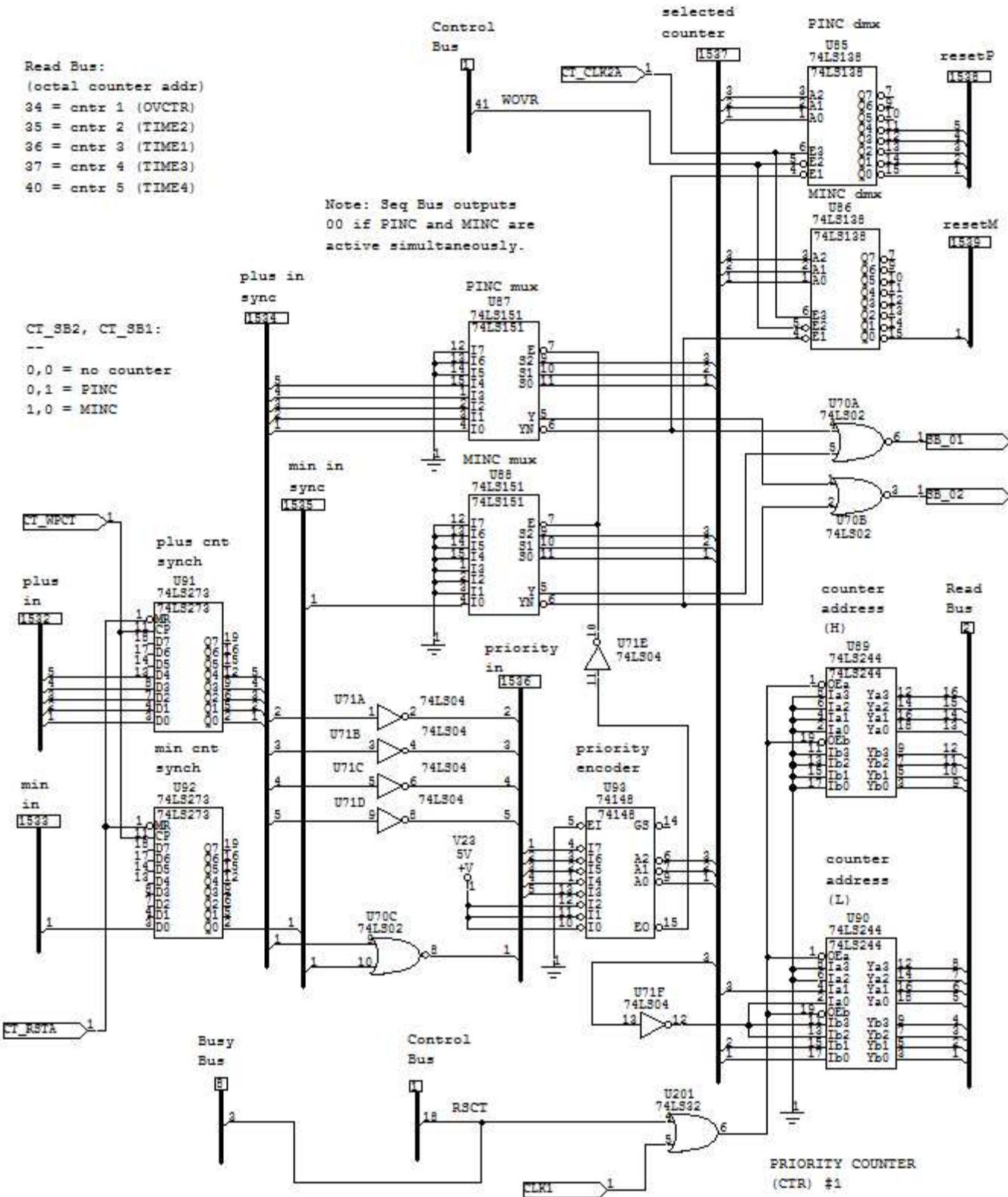

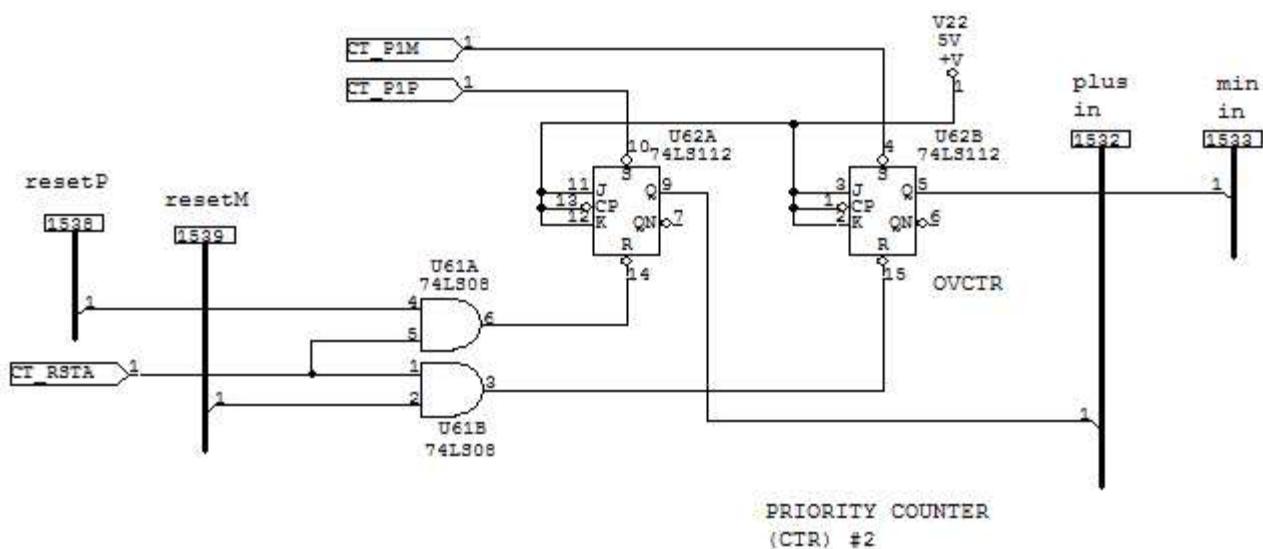

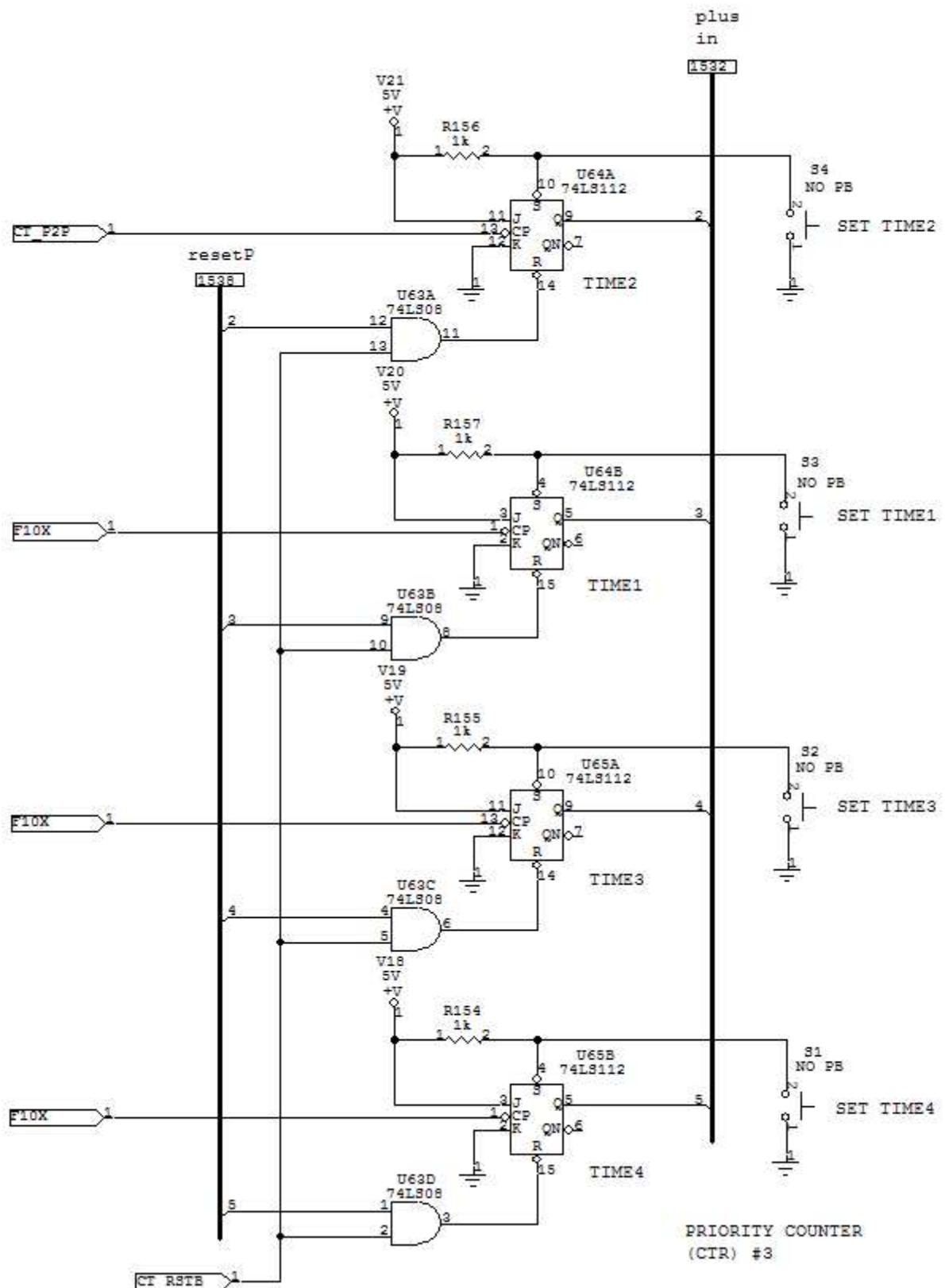

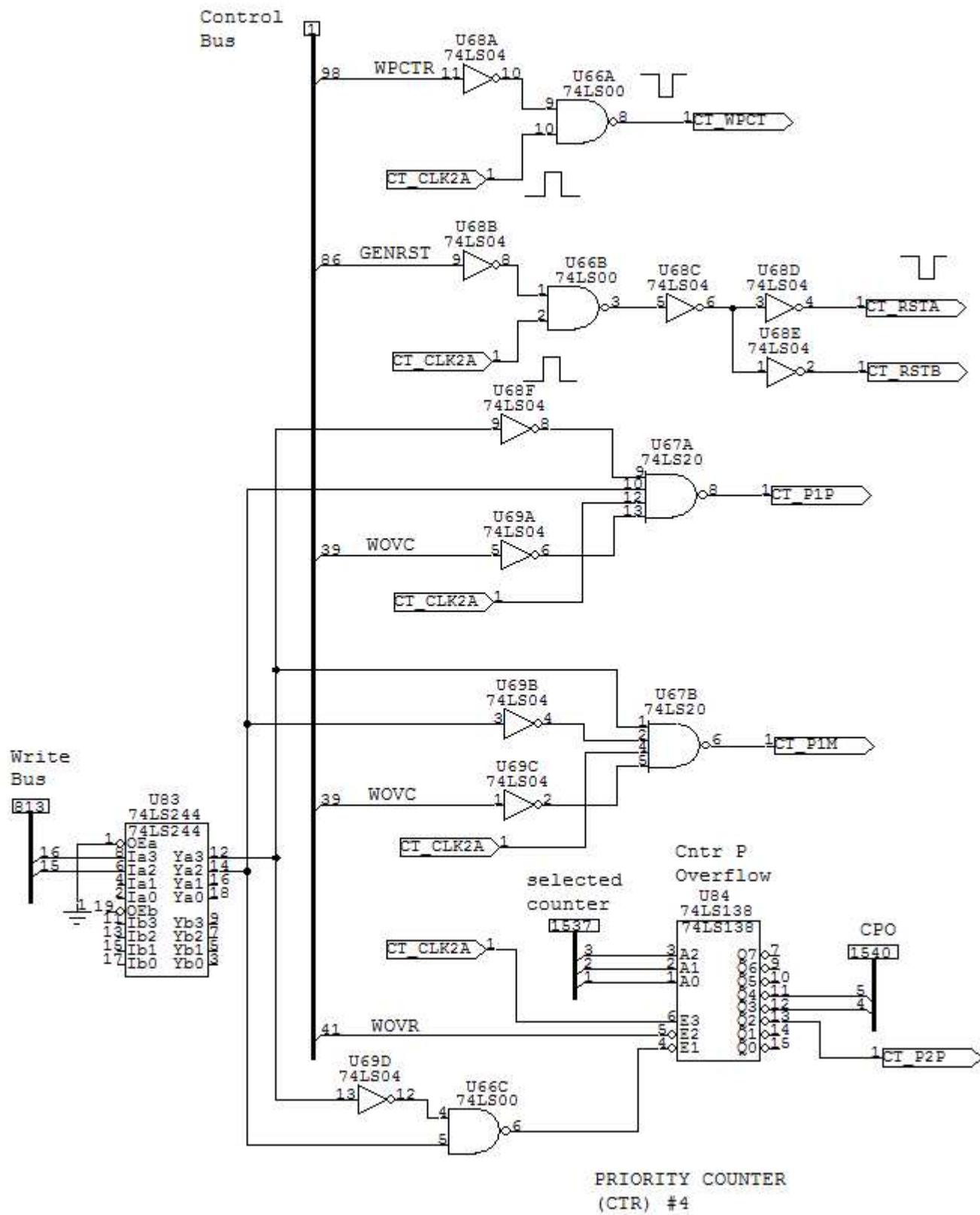

# Fabrication

The PROC module is (4) 13"x5" circuit boards, and 1 control panel.

## Module Rack

The module framework is designed to resemble a relay rack, but scaled to fit the circuit board dimensions. It is constructed out of 1"x2" pine and spray-painted semi-gloss gray.

Circuit boards are mounted to the rack by 2 phillips screws at either end. Nylon spacers (1/4") are used as standoffs to hold the board edges above the rack. The boards are mounted so the chips are in the back and the pins are wiring are visible from the front.


Power is distributed by 2 heavy aluminum bus bars mounted vertically, one per side, on the back of the module. Machine screws are mounted through the bus bars at evenly-spaced intervals to provide connection points for the boards.

Solid copper wire (24 gauge) connects the boards to the bus bars. Ring terminals are used on the bus bar side of the connection. On the circuit board size, the wires are soldered directly to the supply rails.

Materials were purchased from Home Depot, ACE Hardware, and Radio Shack.
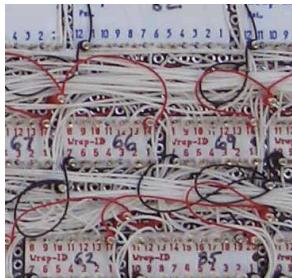
## Circuit Boards


The circuit boards are 13"x5" general purpose prototyping boards, epoxy glass with double-side plated through pads on 0.1" centers (JAMECO 21477CL).



ICs are mounted in level 3 machine tooled wire-wrap sockets: 8, 14, 16, 20, 24, and 28 pin (JAMECO). Each socket has the pin-out labeled with a wire-wrap socket ID marker, which slips onto the socket before wrapping (JAMECO). The part number is written onto the ID marker.

Sockets are arranged in 4 horizontal rows on each board, with about 10 sockets per row.

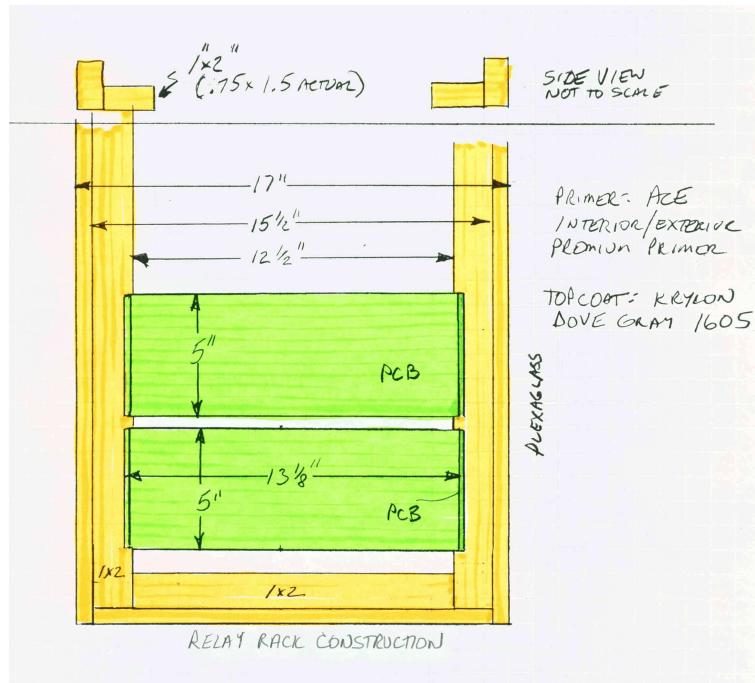Power is distributed on the back-side of each board by bare 24-gauge solid copper wire supply rails soldered at equal intervals to Klipwrap terminals: 3-prong terminals with a square tail for wire-wrapping (JAMECO 34163CL). A +5V rail runs above each row of sockets and a ground rail runs below. Each rail connects directly to the aluminum module power bus using a ring tail connector.



On the pin side of the board, all connections are made with 30 AWG Kynar wire-wrap wire (JAMECO). Red wire is used for direct connections to the +5V supply rail. Black wire is used for direct connections to ground. White wire is used for everything else.


Power connections from the supply rails to each ICs are double-wrapped. Bypassing capacitors (.1 uf disc) are soldered across the supply rails at the Klipwrap terminals; about 1 capacitor for every 2 IC packages.

All connections were stripped and hand-wrapped using a Radio Shack hand-wrap tool. As each connection was made, the corresponding line on the schematic was marked with a colored highlighter.

DIP resistor networks (JAMECO) plugged into 20-pin wire-wrap sockets were used as current limiting resistors for the panel indicators.

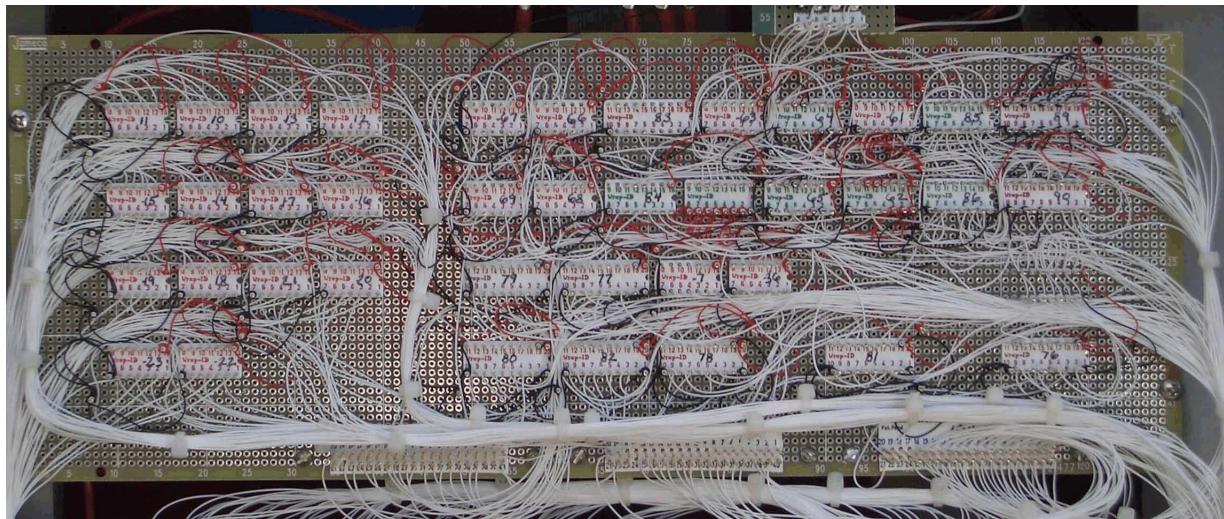
## **PROC Printed Circuit Board (PCB) A**

The A board contains display drivers for the B board (left side), buffers for the interfaces to external modules (bottom right), and priority counter logic (upper right). Sockets for 3 IDE interface cables to external modules are visible at the bottom.



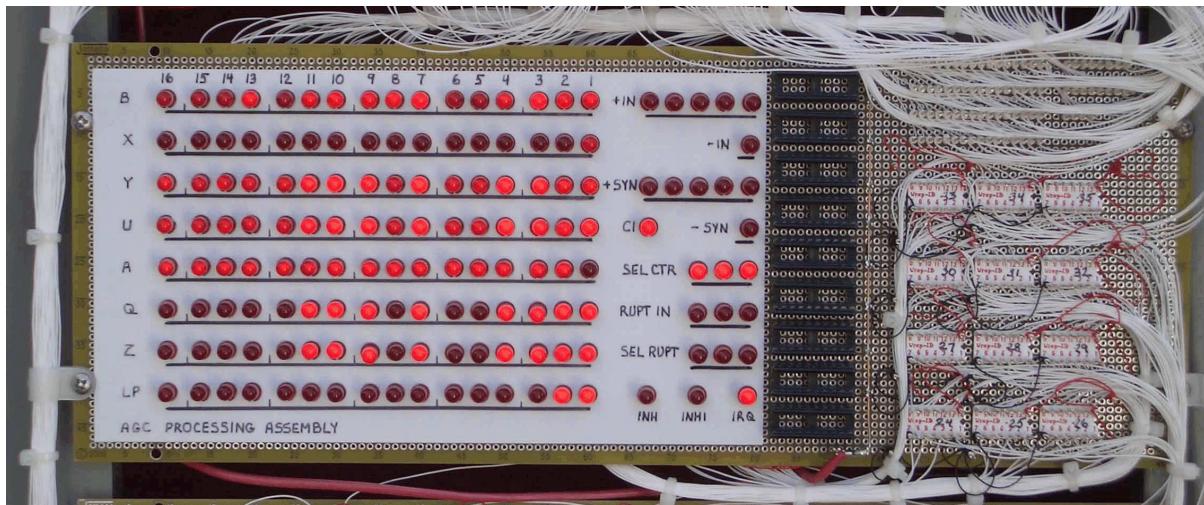
## PROC Printed Circuit Board (PCB) B

The B board contains the display indicators, their current limiting resistor networks, and the open collector drivers. The display panel is a sheet of white styrene plastic. A push pin was used to make holes through the plastic and the LEDs were inserted in rows. The panel was hand-lettered with an indelible marker.



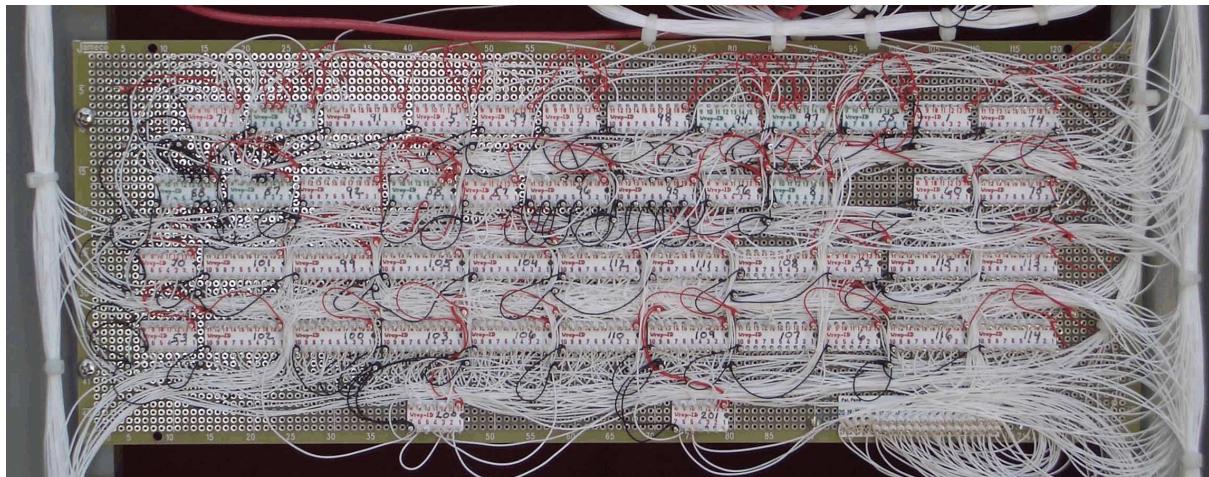
## **PROC Printed Circuit Board (PCB) C**

The C board contains the logic for the interrupt (INT) subsystem (upper half of the board), and the central registers (CRG; lower half of the board).


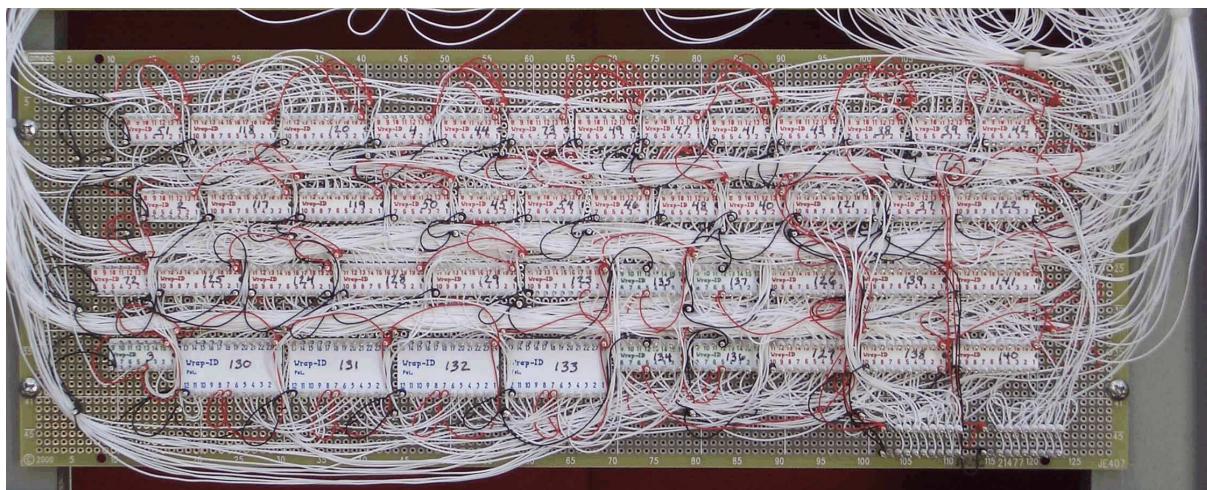
## **PROC Printed Circuit Board (PCB) D**

The D board contains the ALU logic. The large 74181 ALU chips are at the bottom right. The four chips that form the ADDER are in the bottom half of the board, slightly to the right of the middle.



## Parts (ICs)

IC's, sockets, PCB's, resistors, capacitors, wire-wrap wire were purchased from JAMECO. IDE wire-wrap sockets were from DigiKey. Wire ties, wire-wrap tools, and copper wire were from Radio Shack. IDE ribbon cables were purchased from an online computer supplier.

|         |      |  |
|---------|------|--|
| 74LS00  | (9)  | U60,U66,U57,U53,U51,U44,U46,U47,U42  |
| 74LS02  | (4)  | U70,U6,U49,U2  |
| 74LS04  | (11) | U54,U45,U37,U68,U7,U36,U69,U71,U59,U48,U72   |
| 74LS06  | (26) | U28,U29,U30,U31,U27,U26,U23,U24,U25,U22,U21,U20,U18,U19,U17,U<br>16,U15,U12,U13,U14,U11,U10,U35,U34,U33,U32  |
| 74LS08  | (4)  | U63,U61,U56,U52  |
| 74LS10  | (2)  | U50,U43  |
| 74LS20  | (2)  | U67,U73  |
| 74LS21  | (1)  | U1   |
| 74LS27  | (1)  | U9   |
| 74LS32  | (5)  | U4,U41,U40,U39,U38   |
| 74LS83  | (4)  | U134,U135,U136,U137  |
| 74LS86  | (1)  | U5   |
| 74LS112 | (7)  | U65,U64,U62,U58,U55,U8,U3  |
| 74LS138 | (4)  | U84,U85,U86,U94  |
| 74LS148 | (2)  | U93,U97  |
| 74LS151 | (2)  | U87,U88  |
| 74LS181 | (4)  | U130,U131,U132,U133  |
| 74LS244 | (33) | U74,U75,U76,U77,U78,U79,U80,U81,U82,U83,U89,U90,U95,U96,U101,<br>U102,U104,U105,U108,U111,U112,U115,U116,U117,U118,U119,U120,<br>U121,U122,U124,U125,U128,U129 |
| 74LS273 | (19) | U91,U92,U98,U99,U100,U103,U106,U107,U109,U110,U113,U114,U123<br>,U126,U127,U138,U139,U140,U141   |

## Power Budget

|         | <u>qty</u> | <u>mA (ea)</u> | <u>mA (tot)</u> |
|---------|------------|----------------|-----------------|
| 74LS00  | 9          | 2.4            | 21.6            |
| 74LS02  | 4          | 2.4            | 9.6             |
| 74LS04  | 11         | 3.6            | 39.6            |
| 74LS06  | 26         | 3.6            | 93.6            |
| 74LS08  | 4          | 4.4            | 17.6            |
| 74LS10  | 2          | 1.8            | 3.6             |
| 74LS20  | 2          | 1.2            | 2.4             |
| 74LS21  | 1          | 2.2            | 2.2             |
| 74LS27  | 1          | 3.4            | 3.4             |
| 74LS32  | 5          | 4.9            | 24.5            |
| 74LS83  | 4          | 22.0           | 88.0            |
| 74LS86  | 1          | 6.1            | 6.1             |
| 74LS112 | 7          | 4.0            | 28.0            |
| 74LS138 | 4          | 6.3            | 25.2            |
| 74LS148 | 2          | 12.0           | 24.0            |
| 74LS151 | 2          | 6.0            | 12.0            |
| 74LS181 | 4          | 21.0           | 84.0            |
| 74LS244 | 33         | 32.0           | 1056.0          |

|         |     |                       |        |
|---------|-----|-----------------------|--------|
| 74LS273 | 19  | 17.0                  | 323.0  |
| LED     | 153 | 20.0                  | 3060.0 |
| -----   |     |                       |        |
|         | 4.9 | Amps total            |        |
|         | 1.9 | Amps (excluding LEDs) |        |